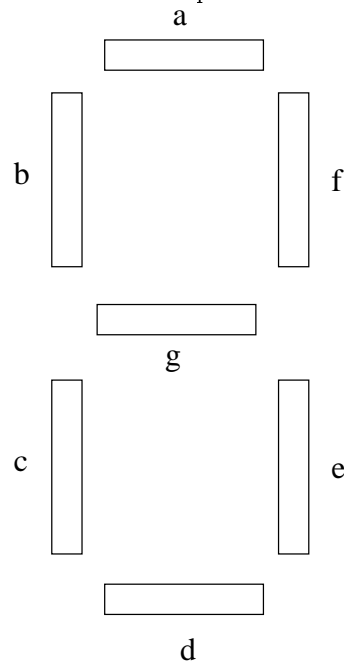


Asssignment 2

Problem: Design a BCD to 7-Segment LED Display Driver. Assume that when LED-'a' is glowing the value corresponding to 'a' is HIGH. Formulate the boolean functions for a, b, c, d, e, f, g. and design the driver in 180nm technology using

- 1) Static CMOS.
 - 2) Pass Transistor Logic (Using LEAP Cells).
 - 3) Using Dynamic CMOS Logic (Domino Logic).
- Assume 4 bit inputs and values above 9 are all don't care.



Those who have access to DOE lab, can do the same using their technology.

SUBMISSION DEADLINE: Before Mid-Sem (23rd Feb).