

Submission date: 7th August 2018

Submission procedure: Take the snapshot of the schematic and save the waveforms and prepare a word document. Add comments/discussion wherever required. The whole report should not exceed six pages. Submit the hard-copy/print-out version of the report.

1. A current mirror circuit is shown in Figure 1 where $I_{in}=100\ \mu A$.
 - a. Find out the threshold voltage of the transistors.
 - b. If each transistor has $W/L = 10\mu m/0.5\mu m$, measure the value of I_{out} .
 - c. After that, increase the transistor size $100\mu m/5\mu m$ and measure the value of I_{out} .
 - d. Are there any differences you see in the results in step (b) and step (c)? Comment.

 


Figure 1

2. Design an NMOS differential pair with resistive load (shown in Figure 2) for a voltage gain of 50 and a power budget of $200\ \mu W$ subject to the condition that the stage following the differential pair an input CM level of at least $1.2V$.

 


Figure 2

3. A differential amplifier with an active current mirror load (shown in Figure 3) has a tail bias current of $200\ \mu\text{A}$. All the transistors have $W/L = 20\mu\text{m}/0.4\mu\text{m}$. Assume the input common mode voltage of $1.2\ \text{V}$ and $R_L = 10\ \text{k}\Omega$.
- Find out the differential gain of the circuit.
 - Find out the output common mode range.

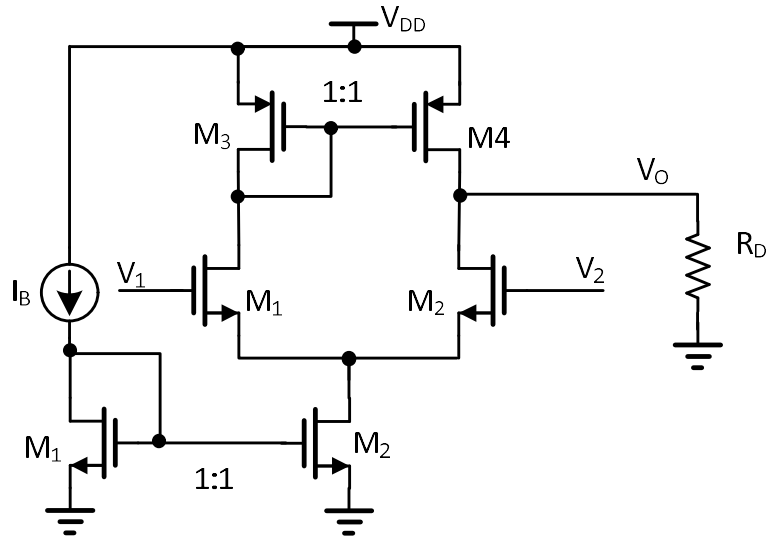


Figure 3