

- Find the resolution for a DAC if the output voltage is desired to change in 1 mV increments while using a reference voltage of 5V. [Ans: 13 bits]
- From any non-ideal characteristics of the converter, find out INL and DNL. [One example has been shown in the class.]
- A full scale sinusoidal waveform is applied to a 12 bit ADC and the output is digitally analyzed. If the fundamental has a normalized power of 9 W while the remaining noise power is 0.5 μ W, what is the effective number of bits of the converter? [Ans: 10.2 bits]
- An 8-bit ADC has a reference voltage $V_{ref}=4V$. Find the RMS value of the quantization noise. Also find SNR of the ADC for full scale sine wave input and half scale sine wave input.
- To a serial charge redistribution DAC, the word 1101 is applied to convert as an analog output. Follow through the sequence of events that result in conversion of this digital input word. [Solved in the class]
- Assume that the sampled analog input to a 4-bit pipeline algorithmic ADC is 2.0 V. If V_{ref} is 5 V, find the digital output word and the analog equivalent voltage. [Solved in the class]
- Assume $M=2$ and $K=2$, find out the transfer characteristic of this DAC if the scaling factor of the LSB sub-DAC is $3/8$ instead of $1/4$. Assume $V_{ref}=1$ V. What is the $\pm INL$ and $\pm DNL$ for this DAC? Is this DAC monotonic? [Ans: $INL=1.5LSB$, $DNL=-1.5LSB$]

