


 
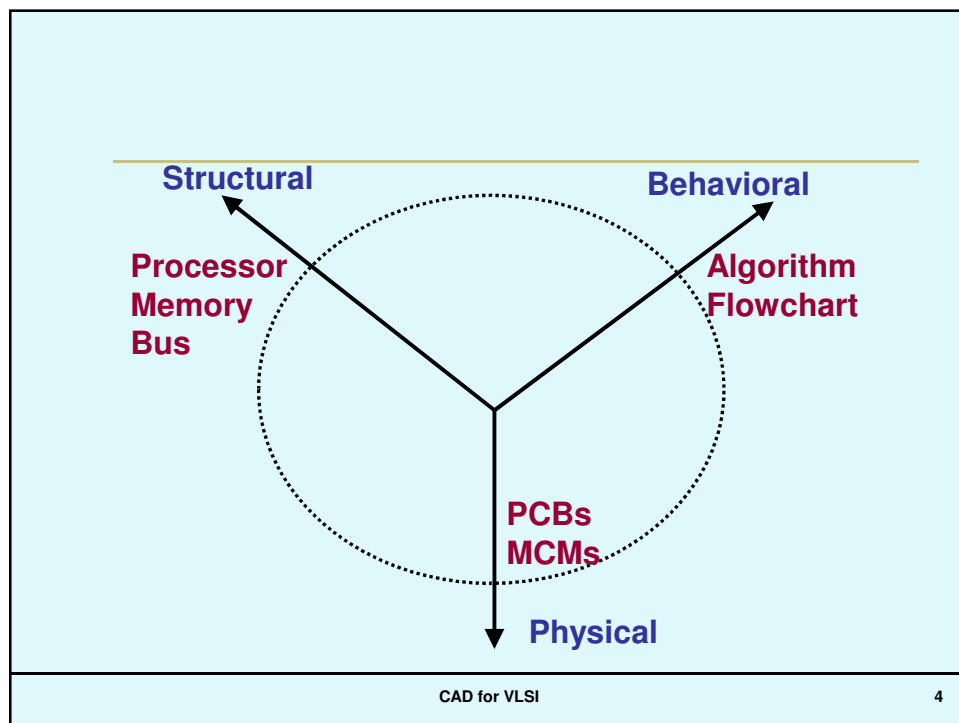




Synthesis

The Y-diagram Revisited

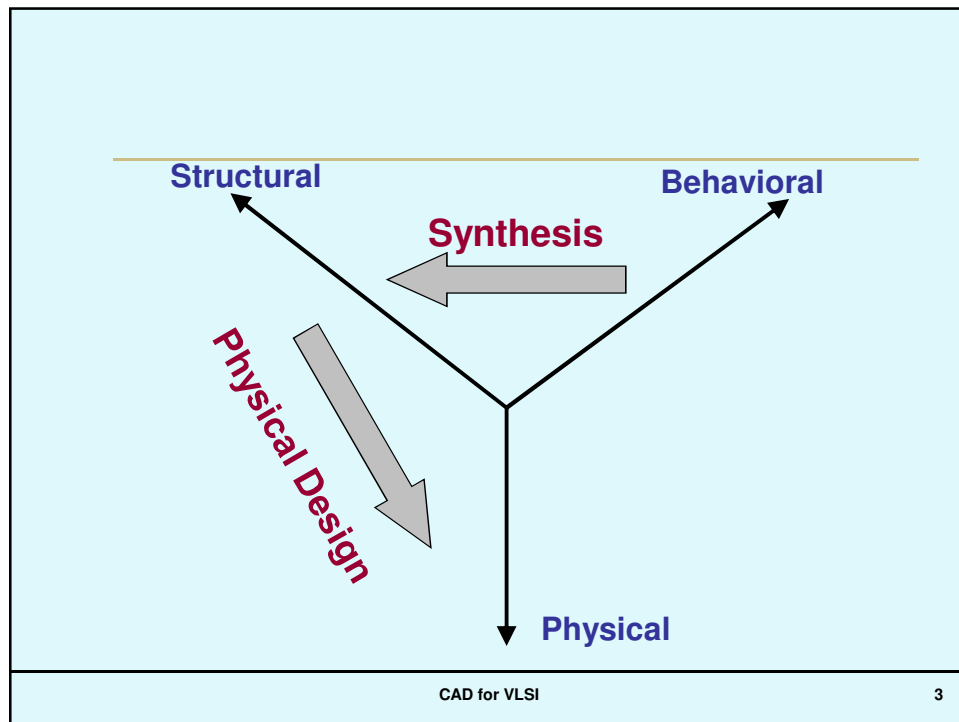

 

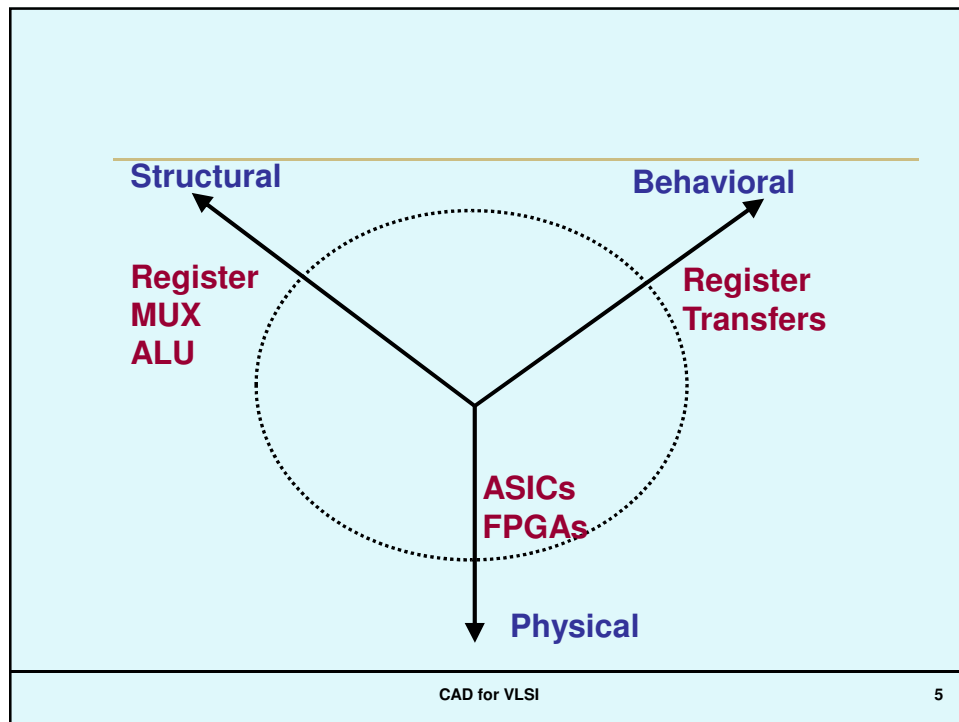

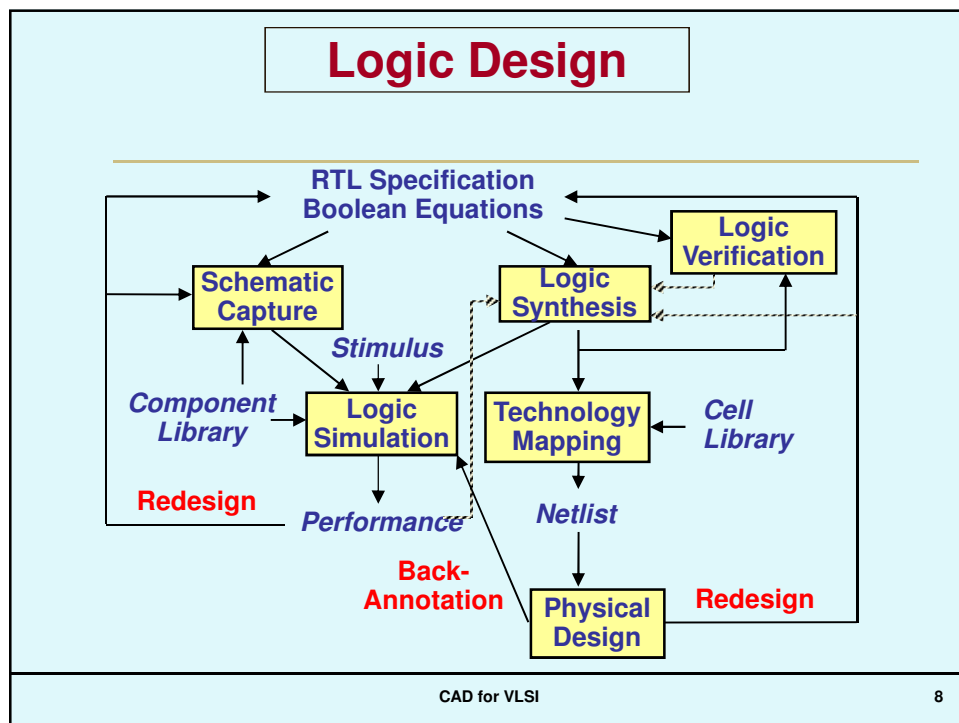 


Schematic Capture

- **Schematic**
 - Graphical representation of a netlist of components.
- **Schematic Capture**
 - Interactive creation of a schematic
 - Using a schematic editor
 - Uses component icons
 - Picks up components from library
 - Creates netlist
 - Input to simulation & synthesis tools

CAD for VLSI

9

Schematic

 

Netlist

nand2	1	2	3
nand2	1	3	4
nand2	2	3	5
nand2	4	5	6

CAD for VLSI

10

Logic Simulation

- Takes a logic level netlist as input, and simulate functional behavior.
 - “Netlist” obtained from schematic capture or synthesis.
 - For simulation, the behavior of components is used.
 - Available from component library
 - Gates, flip-flops, MUX, registers, adder
- Ability to handle large circuits (millions of gates)
 - Should be very fast
 - Hardware accelerators

CAD for VLSI

11

- Simulation Objectives
 - Functional correctness of the netlist
 - Requires application of a set of test vectors → test bench
 - Timing analysis
 - Estimation of delay, critical paths
 - Hazards, races, etc.
 - Test generation
 - Required for manufacture test
 - To be discussed later

CAD for VLSI

12

Logic Synthesis

- Input: Boolean equations and FSMs
- Output: A netlist of gates and flip-flops
 - Combinational circuits and sequential circuits are typically handled separately
- Design Goals:
 - Minimize number of levels (delay)
 - Minimize number of gates (area)
 - Minimize signal activity (power)
- Typical Constraints:
 - Target library (say, only NAND and NOT gates)

CAD for VLSI

13

- Special Considerations
 - Ability to handle large circuits within a reasonable amount of time.
 - Problem is known to be NP-complete
 - Ability to handle mutually conflicting requirements (area & delay)
 - Typically a fully automated process
 - Algorithms/heuristics well understood
 - Do not need user intervention
 - Use technology dependent considerations
 - Break a 20-input gate into smaller gates
 - Use gates available in the library

CAD for VLSI

14


Technology Mapping

- **Basic Concept:**
 - During logic synthesis, map portions of the netlist to “cells” available in the cell library
 - Standard library (NAND, NOR, NOT, AOI, etc)
 - FPGA cells, standard cells
- **Objectives:**
 - Minimize area, delay, power
 - Should be fast
 - Able to handle large circuits, and large technology libraries

CAD for VLSI

15

An Example

 

CAD for VLSI

16

Logic Verification

- **Verify that the synthesized netlist matches the original specification**
 - Detect design errors, also synthesis errors
 - Basic objective is to ensure functional correctness, and to locate errors, if any
- **Broadly two approaches:**
 1. Simulation
 - Fast, incremental, can handle large circuits
 2. Formal verification
 - Slow, exhaustive, for small circuits only

CAD for VLSI



17

Logic Synthesis

The Basic Problem

- Convert from logic equations to gate-level netlists (assume combinational logic).
 - Maximize speed
 - Minimize area, power

$$a'bc + abc + d \rightarrow bc + d$$

  

CAD for VLSI

19

Logic Specification

• PLA Format

```
.i 3
.o 3
.p 4
1x1 011
x00 010
1x0 100
x11 011
.e
```

• Sum-of-product form

$$\begin{aligned} x &= ac' \\ y &= ac + b'c' + bc \\ z &= ac + bc \end{aligned}$$

CAD for VLSI

20

Logic Synthesis Problem

1. **Simplification of logic equations**
 - Reduce number of literals (and operands)
2. **Synthesis**
 - Map logic equations to gates (AND, OR, etc)
3. **Gate-level optimization**
 - Replace OR-NOT by NOR, for example
 - Delay, power, area
4. **Technology mapping**
 - Map from gates to technology library
 - FPGA, TTL chips, standard cells, etc

CAD for VLSI

21

Two Level Logic Minimization

Basic Approaches

- **Karnaugh Maps**
 - For n inputs, the map contains 2^n entries
 - Objective is to find minimum prime cover
 - Minimum → fewest terms
 - Prime → choose only maximal covers
 - Don't care terms are used to advantage
 - Difficult to automate
 - Minimum cover problem is NP-complete
 - Process can get into a local minima

CAD for VLSI

23

- **Problems with K-maps:**
 - Number of cells is exponential in the number of input variables.
 - Imagine a 50-input circuit
 - Requires efficient data structures
 - For representing the function
 - For searching for minimal prime cover
 - Quine-McCluskey method
 - Easy to implement in software
 - Computational complexity remains high

CAD for VLSI

24


Espresso: A 2-level logic optimizer

- Some notations:
 - For an n -input function, n -dimensional Boolean space
 - Each point mapped to a unique combination of the n literals
 - Entries in K-map, minterm
 - Cube
 - Conjunction (AND) of literals in an n -dimensional space
 - Points on the n -dimensional hypercube that are “1”

CAD for VLSI

25

 - Expression
 - Disjunction (OR) of cubes
- Don't cares
 - Literals that are missing from a cube



CAD for VLSI

26

- **Basic Approach**

- Minimize cover of “ON-set” of the function
 - ON-set → set of vertices that correspond to “1” minterms
 - Minimum set of cubes
 - Size of the cubes can be increased by exploiting don’t care literals

CAD for VLSI

27

- **The Espresso Algorithm (Outline)**

- Start with the sum-of-products form (i.e., cubes covering the ON-set).
- Expand, remove redundancy (irredundant) and reduce cubes in an iterative loop, until no further improvement is possible.
- Perturb the solution, and repeat the previous iterative steps, as long as the time budget permits.
 - For each cube, add a subcube not covered by any other cube.
 - Expand subcubes and add them if they cover another cube.

CAD for VLSI

28

ESPRESSO Algorithm

```

Forig = ON-set;           /* vertices with expression TRUE */
R = OFF-set;              /* vertices with expression FALSE */
D = DC-set;               /* vertices with expression DC */
F = expand(Forig, R);      /* expand cubes against OFF-set */
F = irredundant(F, D);     /* remove redundant cubes */
do {
  do {
    F = reduce(F, D);      /* shrink cubes against ON-set */
    F = expand(F, R);
    F = irredundant(F, D);
  } until cost is "stable";
  /* perturb solution */
  G = reduce_gasp(F, D);   /* add cubes that can be reduced */
  G = expand_gasp(G, R);   /* expand cubes that cover another */
  F = irredundant(F+G, D);
} until time is up;
ok = verify(F, Forig, D); /* check that result is correct */

```

CAD for VLSI

29

Cube operation :: expand

- **Make each cube as large as possible without covering a point in the OFF-set.**
 - Increases the number of literals in the cover.
 - Sets the stage for finding a new and possibly better solution.
- **Example:**


$$f = a'bc' + bc + ab'c'$$

Don't care: $ab'c$ 

$$f = a'b + bc + ac + ab'$$

CAD for VLSI

30

 

Cube operation :: irredundant


- **Throw out redundant cubes.**
 - Points may be covered by several cubes after the 'expand' step.
 - Remove smaller cubes whose points are covered by larger cubes.
 - There must be one cube for every essential vertex.
- **Example:**

$$f = a'b + bc + ac + ab'$$



$$f = a'b + ac + ab'$$

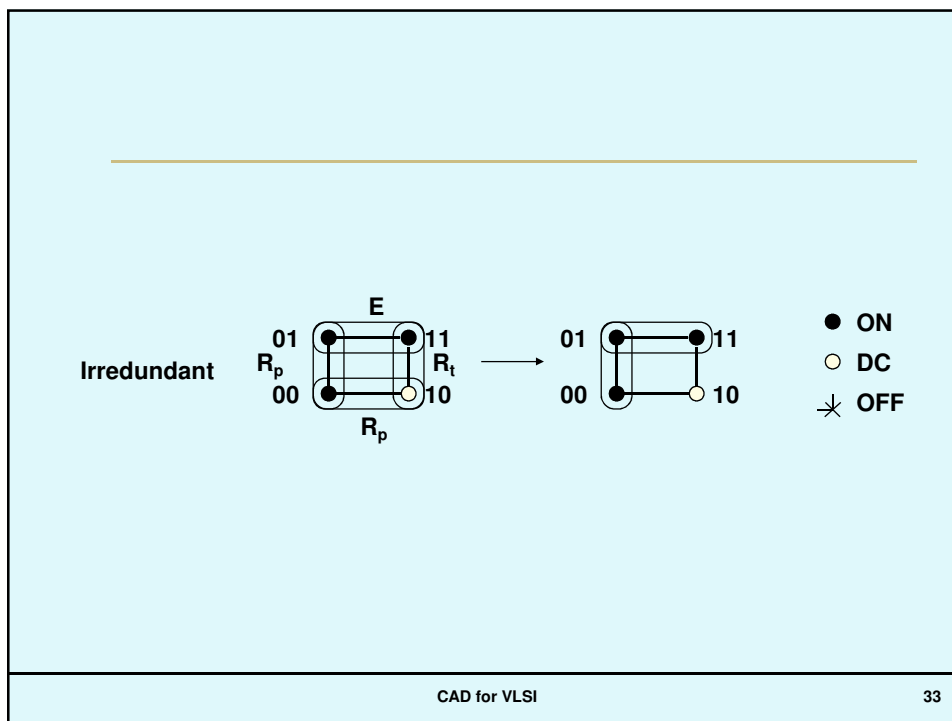One vertex in bc
is covered by $a'b$
& the other by ac



Cube operation :: reduce


- The cubes in the cover are reduced in size.
 - The number of literals in the cover is reduced.
 - Smaller cubes can expand in more directions.
 - Smaller cubes are more likely to be covered by other cubes during expansion.

- Example

$$f = a'b + ac + ab'$$



$$f = a'b + abc + ab'c'$$

 


- In general, the new cover will be different from the initial cover.
 - “expand” and “irredundant” steps can possibly find out a new way to cover the points in the ON-set.
 - Hopefully, the new cover will be smaller.
- CAD for VLSI 36

Cube operation :: perturbations

- **Reduce Gasp**
 - For each cube add a subcube not covered by other cubes.
- **Expand Gasp**
 - Expand subcubes and add them if they cover another cube.
 - Later use “irredundant” to discard redundant cubes.
 - This is a “last gasp” heuristic for exploration.
 - No ordering of cube size.

CAD for VLSI

37

 

CAD for VLSI

38

• Example:

$$f = a' + b \rightarrow f = a' + b + a'b' + ab$$

(Reduce Gasp)


$$f = a'b' + a'b + \textcircled{ab} \rightarrow f = a'b' + a'b + b$$

(Expand Gasp)

CAD for VLSI


39

An example

 

CAD for VLSI

40

 


Espresso :: conclusion

- The algorithm successively generates new covers until no further improvement is possible.
- Produces near-optimal solutions.
- Used for PLA minimization, or as a sub-function in multilevel logic minimization.
- Can process very large circuits.
 - 10,000 literals, 100 inputs, 100 outputs
 - Less than 15 minutes on a high-speed workstation

Multi Level Logic Minimization

Motivation

 - In many applications, 2-level logic is unsuitable as compared to random (multilevel) logic.
 - Gates with high fanin are slow, and take more area.
 - It makes sense to transform a 2-level logic realization to multi-level logic.



- **A classical example :: XOR function**

- For an 8-input XOR function,

- For 2-level NAND-NAND realization

$${}^8C_1 + {}^8C_3 + {}^8C_5 + {}^8C_7 = 128 \text{ NAND8 gates}$$

1 NAND128 gate

- For 3-level XOR realization

7 XOR2 gates

→ 28 NAND2 gates

Number of levels = 9

CAD for VLSI

45

- **Multilevel logic optimization approaches:**

1. Local optimization

- » Rule-based transformation

2. Global optimization

- » Weak division

CAD for VLSI

46

Local Optimization Technique

- Used in IBM Logic Synthesis System.
- Perform rule-based local transformations.
 - Objective → reduce area, delay, power.
 - Developing a good set of rules is a challenge.
 - Should be comprehensive enough so as to completely explore the design space.
- Basic idea:
 - Apply a transformation which reduces cost.
 - Iterate and continue the transformations as long as solution keeps improving.

CAD for VLSI

47

- **AND/OR transformations**
 - Reduce the size of the circuit, critical path.
 - Typical transformations:
 - $a \cdot 1 = a$
 - $a + 1 = 1$
 - $a + a' = 1$
 - $a \cdot a' = 0$
 - $(a')' = a$
 - $a + a' \cdot b = a + b$
 - $\text{xor}(\text{xor}(a_1, a_2, \dots, a_n), b) = \text{xor}(a_1, a_2, \dots, a_n, b)$
- Transform the AND/OR form to NAND (or NOR) form.

CAD for VLSI

48

- **NAND (NOR) transformations**

- Some synthesis systems assume that all gates are of the same type (NAND or NOR).
- Does not require technology mapping.
- Rules framed that transform one NAND (NOR) network to another.
- Examples:

$$\text{NAND}(\text{NOT}(\text{NAND}(a,b)), c) = \text{NAND}(a,b,c)$$

$$\text{NAND}(\text{NAND}(a,b,c), \text{NAND}(a,b,c')) = \text{NAND}(a,b)$$

CAD for VLSI

49

How complex is the algorithm?

- $n \rightarrow$ number of circuit nodes
 $m \rightarrow$ number of rules
 - Ordering of rule (by cost reduction) takes $O(mn \log mn)$ time.
 - The process has to be repeated many times.
- To speed up, we can use *lazy evaluation*.
 - We only check those circuit nodes which were modified in the previous iteration.
 - $O(m \log m)$ for every rule application.

CAD for VLSI

50

Global Optimization Technique

- **Used in GE Socrates.**
 - Looks at all the equations at one time.
- **Perform weak division.**
 - Divide out common sub-expressions.
 - Literal count gets reduced.
- **The following iterative steps are carried out:**
 - Generate the candidate sub-expressions.
 - Select a sub-expression to divide.
 - Divide functions by selected sub-expression.

CAD for VLSI

51

Example

- Original equations:

$$f_1 = a.b.c + b.c.d + b.e.g \quad f_2 = b.c.f.h + d.g + a.b.g$$

→ No. of literals = 18

 - We find literals saved for sub-expressions:

$b.c \rightarrow 4$	$a.b \rightarrow 2$
$a + d \rightarrow 2$	$b.g \rightarrow 2$

Select the sub-expression bc.
- Modified equations (after iteration 1):

$$f_1 = (a + d).u + b.e.g$$

$$f_2 = u.f.h + d.g + a.b.g$$

$$u = b.c$$

→ No. of literals = 14+2

CAD for VLSI

52

$$\begin{aligned}f_1 &= (a + d).u + b.e.g \\f_2 &= u.f.h + d.g + a.b.g \\u &= b.c\end{aligned}$$

- Literals saved for the sub-expressions:
b.g → 2

- Modified equations (after iteration 2):

$$\begin{aligned}f_1 &= (a + d).u + e.v \\f_2 &= u.f.h + d.g + a.v \\u &= b.c \\v &= b.g\end{aligned}$$

→ No. of literals = 12+4


- No common sub-expressions → **STOP**

CAD for VLSI

53

About the algorithm

 - Basically a greedy algorithm
 - Can get stuck in local minima.
 - Give a “*push*” to come out of local minima.
 - Like the “gasp” function in Espresso.



- Generation of all candidate expressions is expensive.
 - Some heuristic used.

CAD for VLSI

54

Multilevel Logic Interactive Synthesis System (MIS)

- A very popular & widely used algorithm.
 - Uses factoring of equations.
 - Similar to weak division used in Socrates.
 - The target technology is CMOS gate.
 - Complex gates realizing any complex functions.
 - Example:

$$f' = (a + b + c)$$

$$g' = (a + b) \cdot (d + e + f) \cdot h$$

CAD for VLSI

55

Basic Concept

- For global optimization,
 - Use algebraic factorization to identify common sub-expressions.
 - Avoid exponential search.
- For local optimization,
 - Identify 2-level sub-circuits.
 - Minimize them using Espresso, or some similar approach.

CAD for VLSI

56

Global Optimization Approach

- **Given a netlist of gates**
 - Scan the network.
 - Apply simple heuristics to “clean up” the netlist.
 - Constant propagation
 - Double inverter elimination
 - Espresso minimization of each equation
 - Then proceed for global optimization with a view to minimize area.

CAD for VLSI

57

- Basically an iterative approach.
 - Enumerate all common factors and identify the “best” candidate.
 - Equations themselves may be common factors.
 - Invert an equation if it helps.
 - Factors may show up in the inverted form.
 - Number of literals used to estimate area.
- **Factoring can reduce area.**
 - An equation in simple sum-of-products form can have many literals.
 - Many transistors for CMOS realization.
 - Factoring the equation reduces the number of literals.
 - Reduces number of transistors in CMOS realization.

CAD for VLSI

58

Local Optimization Approach

- Next step is to look at the problem locally.
 - Each equation treated as a complex gate.
 - Optimize two or more gates that share one or more literals.
 - Break a large gate into smaller gates.
 - For each equation, the don't care input set is obtained from the neighborhood gates.
 - Minimized using Espresso.
- Also an iterative step.

Binary Decision Diagrams (BDD)

Introduction

- Representation of Boolean functions
 - Canonical
 - Truth table
 - Karnaugh map
 - Set of minterms
 - Non-Canonical
 - Sum of products
 - Product of sums
 - Factored form
 - Binary Decision Diagram (Proposed by Akers in 1978)

CAD for VLSI

61


What is Binary Decision Diagram?

- A data structure used to represent a Boolean function.
- Represented as a rooted, directed, acyclic graph, which consists of *decision nodes* and two *terminal nodes* (0-terminal and 1-terminal).
 - Each decision node is labeled by a Boolean variable and has two child nodes called *low child*, and *high child*.
 - The edge from a node to a low (high) child represents an assignment of the variable to 0 (1).
- A BDD is said to be *ordered* if different variables appear in the same order on all paths from the root.

CAD for VLSI

62

Example

 

CAD for VLSI

63

- Construction of a BDD is based on the *Shannon expansion* of a function.



CAD for VLSI

64

Shannon Expansion

- Given a Boolean function $f(x_1, x_2, \dots, x_i, \dots, x_n)$

- Positive cofactor

$$f_i^1 = f(x_1, x_2, \dots, 1, \dots, x_n)$$

- Negative cofactor

$$f_i^0 = f(x_1, x_2, \dots, 0, \dots, x_n)$$

- Shannon's expansion theorem states that

$$f = x_i' f_i^0 + x_i f_i^1$$

$$f = (x_i + f_i^0)(x_i' + f_i^1)$$

CAD for VLSI


65

How to construct BDD?

$$f = ac + bc + a'b'c'$$

$$= a'(b'c' + bc) + a(c + bc)$$

$$= a'(b'c' + bc) + a(c)$$

 

This is the first step. The process is continued for all input variables.

CAD for VLSI

66

$$f = ac + bc + a'b'c'$$

$$= a'(b'c' + bc) + a(c + bc)$$

$$= a'(b'c' + bc) + a(c)$$

Expand by a

Expand by b

Expand by c


$$b'(c') + b(c)$$

$$b'(c) + b(c)$$

$$c'(1) + c(0) \quad c'(0) + c(1) \quad c'(0) + c(1) \quad c'(0) + c(1)$$

Variable ordering: a, b, c

CAD for VLSI 67

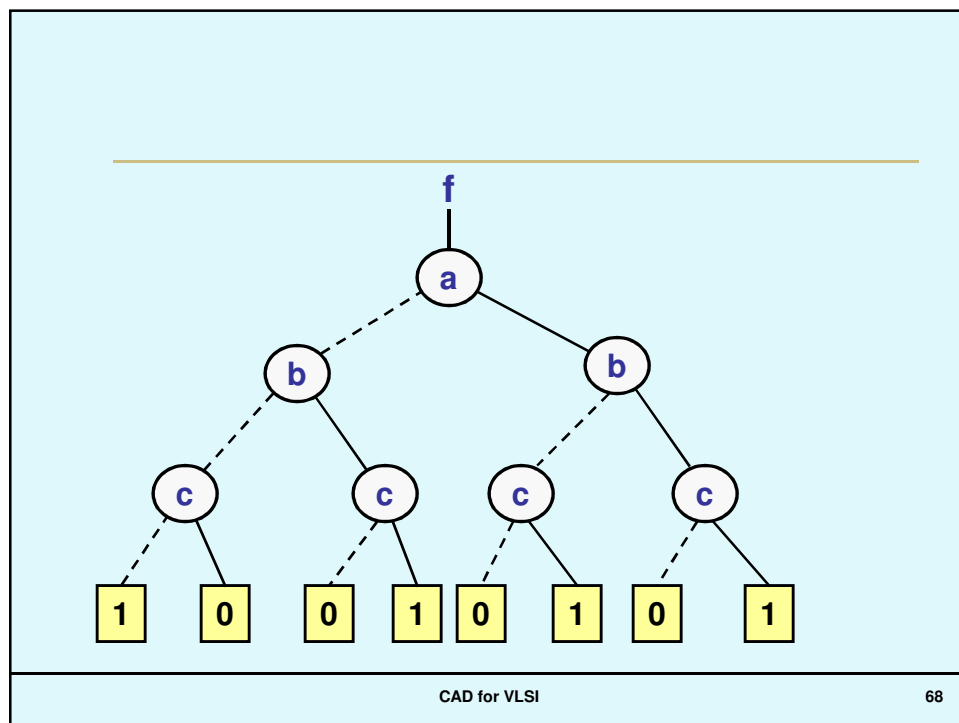

Variable Ordering (OBDD)

- The size of a BDD is determined both by the function being represented and the chosen ordering of the variables.
 - For some functions, the size of a BDD may vary between a *linear* to an *exponential* range depending upon the ordering of the variables.
- An example:

$$f(x_1, \dots, x_{2n}) = x_1x_2 + x_3x_4 + \dots + x_{2n-1}x_{2n}$$

Variable ordering: $x_1 < x_3 < \dots < x_{2n-1} < x_2 < x_4 < \dots < x_{2n}$

BDD requires 2^{n+1} nodes to represent the function.


Variable ordering: $x_1 < x_2 < x_3 < x_4 < \dots < x_{2n-1} < x_{2n}$

BDD requires $2n$ nodes to represent the function.

CAD for VLSI

69

 
BDD for the function $f(x_1, \dots, x_8) = x_1x_2 + x_3x_4 + x_5x_6 + x_7x_8$
using bad variable ordering



CAD for VLSI

70

 Same function using good variable ordering



CAD for VLSI

71

- **Important point to note:**

- It is essential to find a good variable ordering when using the OBDD data structure in practice.
- The problem of finding the best variable ordering is NP-hard.
- Several heuristics for variable ordering have been proposed.

CAD for VLSI

72


Reduced Ordered BDD (ROBDD)

- An ordered binary decision diagram is said to be reduced (ROBDD) if the following two graph reduction rules are applied:
 - Merge any isomorphic subgraphs.
 - Eliminate any node whose two children are isomorphic.
- The advantage of an ROBDD is that it is canonical (unique) for a given function.
 - This property makes it useful in functional equivalence checking.

CAD for VLSI

73


Some Reduction Rules

 

CAD for VLSI

74


Some Reduction Rules (contd.)

 

CAD for VLSI


75

Construction of ROBDD: an example

 

CAD for VLSI

76

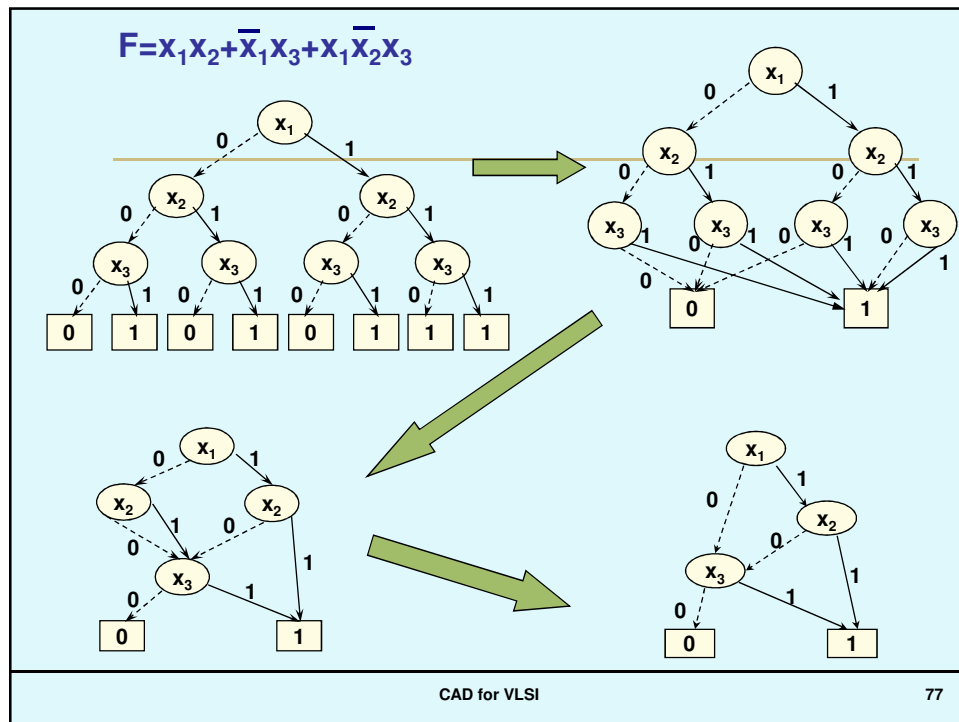


Some Benefits of BDD

- **Checking for tautology is trivial.**
 - BDD is a constant 1.
- **Complementation.**
 - Given a BDD for a function f , the BDD for f' can be obtained by simply interchanging the terminal nodes.
- **Equivalence check.**
 - Two functions f and g are equivalent if their BDDs (under the same variable ordering) are the same.

Use of BDD in Synthesis

 - BDD is canonical for a given variable ordering.
- It implicitly uses factored representation:



CAD for VLSI


79

- Variable reordering can reduce the size of BDD.
 - Implicit logic minimization.
- Some redundancy is also removed during the construction of BDD itself.

CAD for VLSI

80


MUX realization of functions

 

CAD for VLSI

81


MUX-based Functional Decomposition

 

An example ==>

CAD for VLSI

82

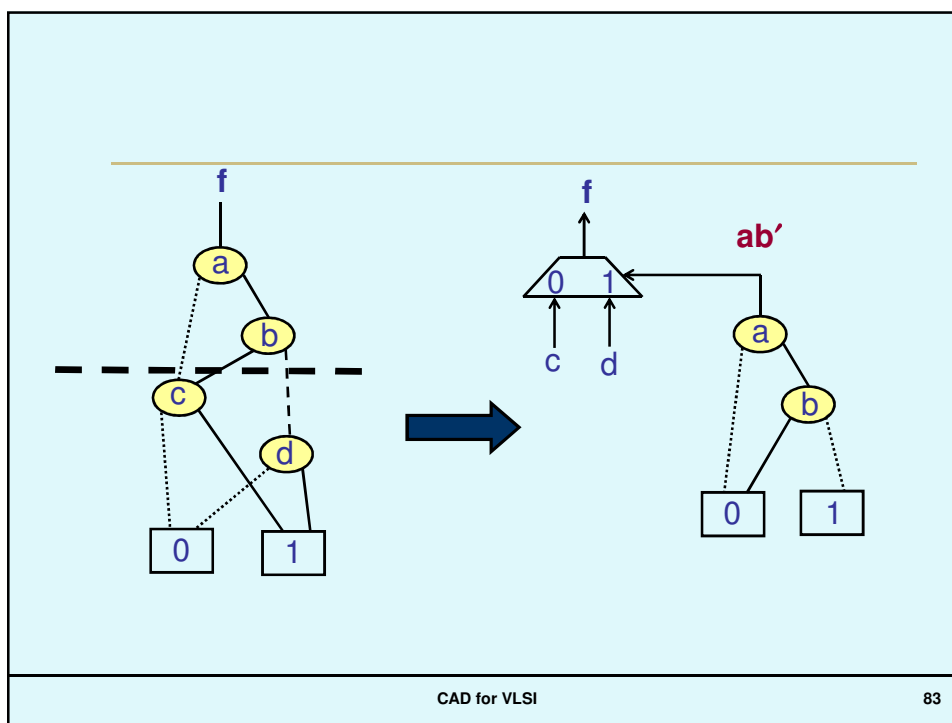

CAD for VLSI

83

To Summarize

- BDDs have been used traditionally to represent and manipulate Boolean functions.
 - Used in synthesis systems.
 - Used in formal verification tools.
 - Efficient packages to manipulate BDDs are available.

CAD for VLSI

84