

Logical Design

Zvi Kohavi and Niraj K. Jha

1

Design with Basic Logic Gates

Logic gates: perform logical operations on input signals

Positive (negative) logic polarity: constant 1 (0) denotes a high voltage and constant 0 a low (high) voltage

Synchronous circuits: driven by a clock that produces a train of equally spaced pulses

Asynchronous circuits: are almost free-running and do not depend on a clock; controlled by initiation and completion signals

Fanout: number of gate inputs driven by the output of a single gate

Fanin: bound on the number of inputs a gate can have

Propagation delay: time to propagate a signal through a gate


2

Analysis of Combinational Circuits

Circuit analysis: determine the Boolean function that describes the circuit

- Done by tracing the output of each gate, starting from circuit inputs and continuing towards each circuit output

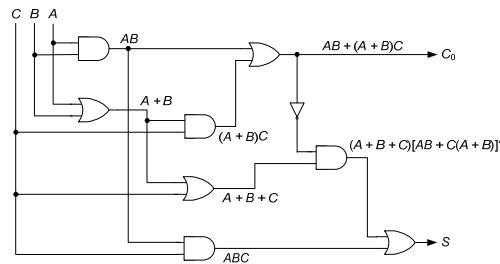Example: a multi-level realization of a full binary adder



$$C_0 = AB + (A + B)C$$

$$= AB + AC + BC$$

$$S = (A + B + C)[AB + (A + B)C]' + ABC$$

$$= (A + B + C)(A' + B')(A' + C)(B' + C) + ABC$$

$$= AB'C' + A'BC' + A'B'C + ABC$$

$$= A \oplus B \oplus C$$


3

Simple Design Problems

Parallel parity-bit generator: produces output value 1 if and only if an odd number of its inputs have value 1

xy \ z	00	01	11	10
0	0	1	0	1
1	1	0	1	0

(a) Map.

 

(b) Implementation.


$$P = x'y'z + x'yz' + xy'z' + xyz$$

4

Simple Design Problems (Contd.)

Serial-to-parallel converter: distributes a sequence of binary digits on a serial input to a set of different outputs, as specified by external control signals

Control		Output lines				Logic equations
C_1	C_2	L_1	L_2	L_3	L_4	
0	0	x	0	0	0	$L_1 = xC_1'C_2'$
0	1	0	x	0	0	$L_2 = xC_1'C_2$
1	0	0	0	x	0	$L_3 = xC_1C_2'$
1	1	0	0	0	x	$L_4 = xC_1C_2$

 

5

Logic Design with Integrated Circuits

Small scale integration (SSI): integrated circuit packages containing a few gates; e.g., AND, OR, NOT, NAND, NOR, XOR

Medium scale integration (MSI): packages containing up to about 100 gates; e.g., code converters, adders

Large scale integration (LSI): packages containing thousands of gates; arithmetic unit


Very large scale integration (VLSI): packages with millions of gates

6

Comparators

***n*-bit comparator:** compares the magnitude of two numbers *X* and *Y*, and has three outputs f_1 , f_2 , and f_3

 - $f_1 = 1$ iff $X > Y$
- $f_2 = 1$ iff $X = Y$
- $f_3 = 1$ iff $X < Y$




(a) Block diagram.

x_1x_2	y_1y_2	00	01	11	10
00		2	1	1	1
01		3	2	1	1
11		3	3	2	3
10		3	3	1	2

 (b) Map for f_1 , f_2 , and f_3 .

$$\begin{aligned}
 f_1 &= x_1x_2y_2' + x_2y_1'y_2' + x_1y_1' \\
 &= (x_1 + y_1')x_2y_2' + x_1y_1' \\
 f_2 &= x_1'x_2'y_1'y_2' + x_1'x_2y_1'y_2 + \\
 &\quad x_1x_2'y_1'y_2' + x_1x_2y_1y_2 \\
 &= x_1'y_1'(x_2'y_2' + x_2y_2) + \\
 &\quad x_1y_1(x_2'y_2' + x_2y_2) \\
 &= (x_1'y_1' + x_1y_1)(x_2'y_2' + x_2y_2) \\
 f_3 &= x_2'y_1y_2 + x_1'x_2'y_2 + x_1'y_1 \\
 &= x_2'y_2(y_1 + x_1') + x_1'y_1
 \end{aligned}$$




(c) Circuit for f_1 .

7


4-bit/12-bit Comparators

Four-bit comparator: 11 inputs (four for *X*, four for *Y*, and three connected to outputs f_1 , f_2 and f_3 of the preceding stage)

12-bit comparator:

 

(a) A 4-bit comparator.

 

(b) A 12-bit comparator.


8

Data Selectors

Multiplexer: electronic switch that connects one of n inputs to the output

Data selector: application of multiplexer

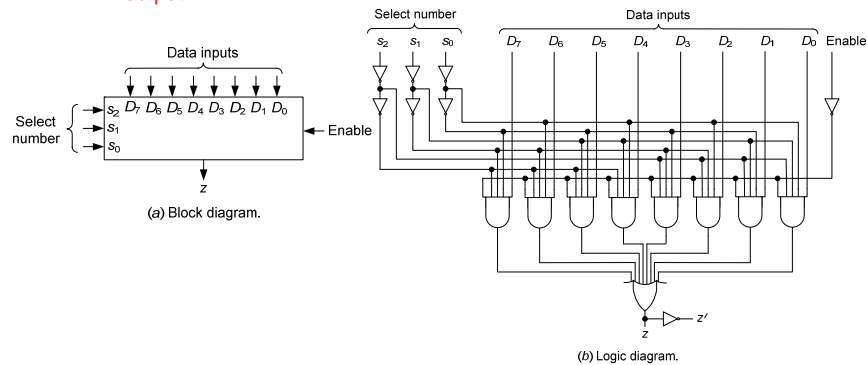- n data input lines, D_0, D_1, \dots, D_{n-1}
- m select digit inputs s_0, s_1, \dots, s_{m-1}
- 1 output




9

Implementing Switching Functions with Data Selectors

Data selectors: can implement arbitrary switching functions

 Example: implementing two-variable functions



$$z = sD_1 + s'D_0$$

If $s = A$, $B = D_0$, and $B' = D_1$, then $z = A \oplus B$.

If $s = A$, $D_0 = 1$, and $D_1 = B'$, then $z = A' + B'$.

10

Implementing Switching Functions with Data Selectors (Contd.)

To implement an n -variable function: a data selector with $n-1$ select inputs and 2^{n-1} data inputs

Implementing three-variable functions:

$$z = s_2's_1'D_0 + s_2's_1D_1 + s_2s_1'D_2 + s_2s_1D_3$$

Example: $s_1 = A, s_2 = B, D_0 = C, D_1 = 1, D_2 = 0, D_3 = C'$

$$\begin{aligned} z &= A'B'C + AB' + ABC' \\ &= AC' + B'C \end{aligned}$$

General case: Assign $n-1$ variables to the select inputs and last variable and constants 0 and 1 to the data inputs such that desired function results


11

Priority Encoders

Priority encoder: n input lines and $\log_2 n$ output lines

- Input lines represent units that may request service
- When inputs p_i and p_j such that $i > j$, request service simultaneously, line p_i has priority over line p_j
- Encoder produces a binary output code indicating which of the input lines requesting service has the highest priority

 Example: Eight-input, three-output priority encoder



(a) Block diagram.

Input lines								Outputs		
p_0	p_1	p_2	p_3	p_4	p_5	p_6	p_7	z_2	z_1	z_0
1	0	0	0	0	0	0	0	0	0	0
φ	1	0	0	0	0	0	0	0	0	1
φ	φ	1	0	0	0	0	0	0	1	0
φ	φ	φ	1	0	0	0	0	0	1	1
φ	φ	φ	φ	1	0	0	0	1	0	0
φ	φ	φ	φ	φ	1	0	0	1	0	1
φ	φ	φ	φ	φ	φ	1	0	1	1	0
φ	φ	φ	φ	φ	φ	φ	1	1	1	1

(b) Truth table.


$$z_2 = p_4p_5p_6p_7' + p_5p_6p_7' + p_6p_7' + p_7 = p_4 + p_5 + p_6 + p_7$$

$$z_1 = p_2p_3p_4p_5p_6p_7' + p_3p_4p_5p_6p_7' + p_6p_7' + p_7 = p_2p_4p_5' + p_3p_4p_5' + p_6 + p_7$$

$$z_0 = p_1p_2p_3p_4p_5p_6p_7' + p_3p_4p_5p_6p_7' + p_5p_6p_7' + p_7 = p_1p_2p_4p_6' + p_3p_4p_6' + p_5p_6' + p_7$$

12

Priority Encoders (Contd.)

 

13


Decoders

Decoders with n inputs and 2^n outputs: for any input combination, only one output is 1

Useful for:

- Routing input data to a specified output line, e.g., in addressing memory
- Basic building blocks for implementing arbitrary switching functions
- Code conversion
- Data distribution


Example: 2-to-4- decoder

 

14

Decoders (Contd.)

 
Example: 4-to-16 decoder made of two 2-to-4 decoders and a gate-switching matrix



15

Decimal Decoder

 
BCD-to-decimal: 4-to-16 decoder made of two 2-to-4 decoders and a gate-switching matrix



(a) Block diagram.

wx		00	01	11	10
yz	00	f_0	f_4	ϕ	f_8
	01	f_1	f_5	ϕ	f_9
	11	f_3	f_7	ϕ	ϕ
	10	f_2	f_6	ϕ	ϕ

(b) Map.

 


(c) Logic diagram.

16

Decimal Decoder (Contd.)

 
Implementation using a partial-gate matrix:



17

Implementing Arbitrary Switching Functions

 Example: Realize a distinct minterm at each output




18


Demultiplexers

Demultiplexers: decoder with 1 data input and n address inputs

 - Directs input to any one of the 2^n outputs




Example: A 4-output demultiplexer

 

19

Seven-segment Display

 Seven-segment display: BCD to seven-segment decoder and seven LEDs



Seven-segment pattern and code:

Decimal digit	BCD code				Seven-segment code						
	x_1	x_2	x_3	x_4	A	B	C	D	E	F	G
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	0	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1
0	0	0	0	0	1	1	1	1	1	1	0

$$A = x_1 + x_2'x_4' + x_2x_4 + x_3x_4$$

$$B = x_2' + x_3'x_4' + x_3x_4$$

$$C = x_2 + x_3' + x_4$$

$$D = x_2'x_4' + x_2'x_3 + x_3x_4' + x_2x_3'x_4$$

$$E = x_2'x_4' + x_3x_4'$$

$$F = x_1 + x_2x_3' + x_2x_4' + x_3'x_4'$$

$$G = x_1 + x_2'x_3 + x_2x_3' + x_3x_4'$$

20


Sine Generators

Combinational sine generators: for fast and repeated evaluation of sine

- Input: angle in radians converted to binary
- Output: sine in binary

Angle x				sin(πx)			
x_1	x_2	x_3	x_4	z_1	z_2	z_3	z_4
0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	1
0	0	1	0	0	1	1	0
0	0	1	1	1	0	0	0
0	1	0	0	1	0	1	1
0	1	0	1	1	1	0	1
0	1	1	0	1	1	1	0
0	1	1	1	1	1	1	1
1	0	0	0	1	1	1	1
1	0	0	1	1	1	1	1
1	0	1	0	1	1	1	0
1	0	1	1	1	1	0	1
1	1	0	0	1	0	1	1
1	1	0	1	1	0	0	0
1	1	1	0	0	1	1	0
1	1	1	1	0	0	1	1

(a) Truth table.

 

$$Z_1 = x_1'x_2 + x_1x_2' + x_2x_3' + x_1'x_3x_4$$

$$Z_2 = x_1x_2' + x_3x_4' + x_1'x_2x_4$$

$$Z_3 = x_3x_4' + x_2x_3 + x_2x_4' +$$

$$x_2'x_3'x_4 + x_1x_4'$$



$$Z_4 = x_2'x_3'x_4 + x_2x_3'x_4' + x_1x_2'x_3' +$$

$$x_1x_3x_4 + x_1'x_2x_4$$

21

NAND/NOR Circuits

  Switching algebra: not directly applicable to NAND/NOR logic




NAND and NOR gate symbols


22

Analysis of NAND/NOR Networks

 Example: circles (inversions) at both ends of a line cancel each other



(a) NAND-logic circuit.

 


(b) Logically equivalent AND-OR circuit.


23

Synthesis of NAND/NOR Networks

Example: Realize $T = w(y+z) + xy'z'$

 

(a) First realization.

 

(b) Realization with two-input gates.

24

Design of High-speed Adders

Full adder: performs binary addition of three binary digits

- Inputs: arguments A and B and carry-in C
- Outputs: sum S and carry-out C_0


Example:

```

0 1 1 = carry-in
1 0 1 1 = augend
0 0 1 1 = addend
-----
1 1 1 0 = sum
    
```

Truth table, block diagram and expressions:

A	B	C	S	C_0
0	0	0	0	0
0	0	1	1	0
0	1	1	0	1
0	1	0	1	0
1	1	0	0	1
1	1	1	1	1
1	0	1	0	1
1	0	0	1	0

 

$$\begin{aligned}
 S &= A'B'C + A'BC' + AB'C' + ABC \\
 &= A \oplus B \oplus C \\
 C_0 &= A'BC + ABC' + AB'C + ABC \\
 &= AB + AC + BC
 \end{aligned}$$


(a) Truth table for S and C_0 .

25

Ripple-carry Adder

Ripple-carry adder: Stages of full adders

 - C_i : forced carry
- $C_{0(n-1)}$: overflow carry



$$\begin{aligned}
 S_i &= A_i \oplus B_i \oplus C_i \\
 C_{0i} &= A_i B_i + A_i C_i + B_i C_i
 \end{aligned}$$

Time required:

- Time per full adder: 2 units
- Time for ripple-carry adder: $2n$ units

26

Carry-lookahead Adder

Carry-lookahead adder: several stages simultaneously examined and their carries generated in parallel

- Generate signal $D_i = A_i B_i$
- Propagate signal $T_i = A_i \oplus B_i$
- Thus, $C_{0i} = D_i + T_i C_i$

To generate carries in parallel: convert recursive form to nonrecursive

$$\begin{aligned}
 C_{0i} &= D_i + T_i C_i \\
 C_i &= C_{0(i-1)} \\
 C_{0i} &= D_i + T_i (D_{i-1} + T_{i-1} C_{i-1}) \\
 &= D_i + T_i D_{i-1} + T_i T_{i-1} (D_{i-2} + T_{i-2} C_{i-2}) \\
 &= D_i + T_i D_{i-1} + T_i T_{i-1} D_{i-2} + T_i T_{i-1} T_{i-2} C_{i-2} \\
 &\dots \\
 C_{0i} &= D_i + T_i D_{i-1} + T_i T_{i-1} D_{i-2} + \dots + T_i T_{i-1} T_{i-2} \dots T_0 C_0
 \end{aligned}$$

Thus, $C_{0i} = 1$ if it has been generated in the i^{th} stage or originated in a preceding stage and propagated to all subsequent stages


27

Carry-lookahead Adder (Contd.)

Implementation of lookahead for the complete adder impractical:

- Divide the n stages into groups
- Full carry lookahead within group
- Ripple carry between groups

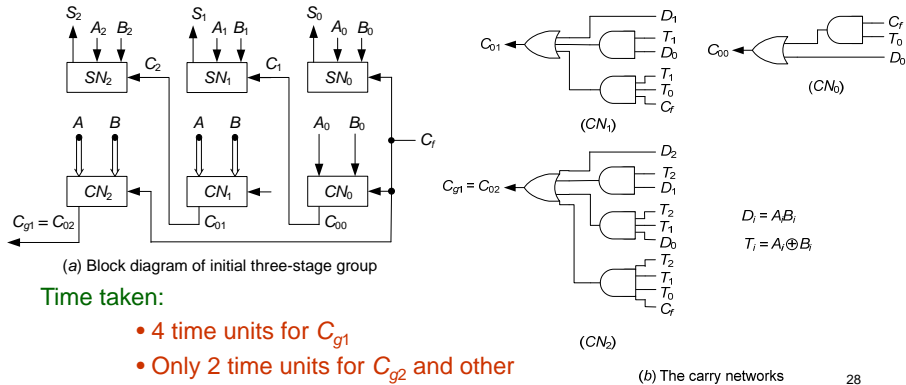
Example: Three-digit adder group with full carry lookahead



30-bit Adder

 Example: divide n stages into groups of three stages

- Time taken: $4 + 2n/3$ time units
- 50% additional hardware for a threefold speedup




29

Metal-oxide Semiconductor (MOS) Transistors and Gates




Complementary metal-oxide semiconductor (CMOS): currently the dominant technology

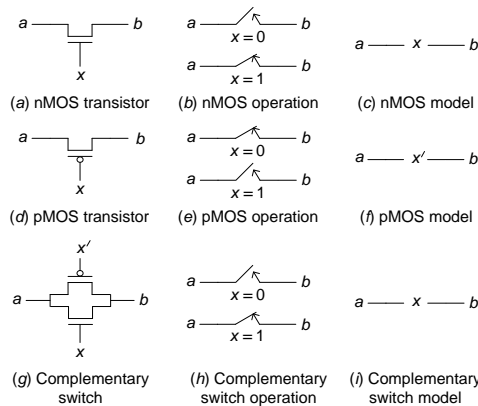- Two types of transistors: nMOS and pMOS




30

Transmission Function of a Network

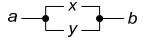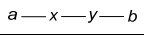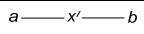
Network	Transmission function
	$T_{ab} = x + y$
	$T_{ab} = xy$
	$T_{ab} = x'$

 CMOS inverter and its transmission functions:




31

CMOS NAND/NOR Gates

 

 (a) CMOS NAND gate and its transmission functions.




(b) CMOS NOR gate and its transmission functions.

32

Analysis of Series-parallel Networks

Algebra of MOS networks: isomorphic to switching algebra

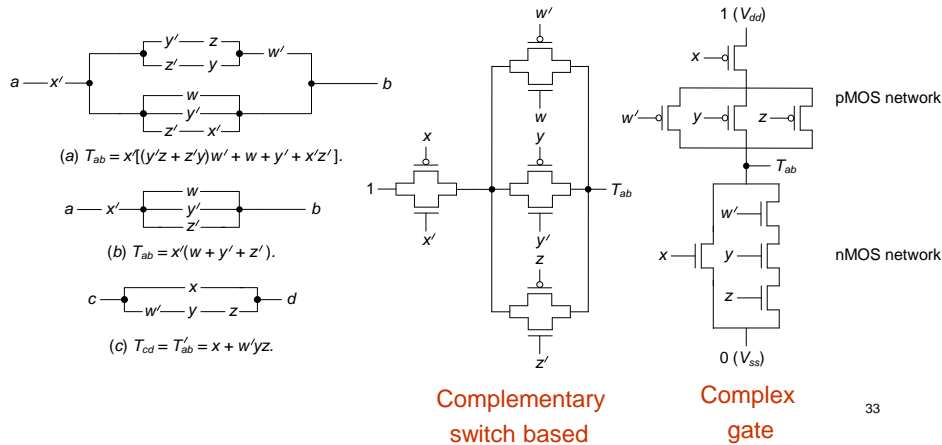
Example: Find the transmission function of the network and its complementary switch based and complex gate CMOS implementations




Analysis of Non-series-parallel Networks

Obtaining the transmission function:

 - Tie sets: minimal paths between two terminals
- Cut sets: minimal sets of branches, when open, ensure no transmission between the two terminals



 (a) Tie sets. $T_{ij} = wx + wvz + yvx + yz$.



(b) Cut sets. $T_{ij} = (w + y)(w + v + z)(x + v + y)(x + z)$.


34

Synthesis of MOS Networks


Sneak paths in non-series-parallel networks: undesired paths that may change the transmission function

- Occur because of bilateral nature of MOS transistors

 
Example: Design a minimal network with BCD inputs that produces a 1 whenever the input is 3 or a multiple of 3



(a) Map for $T = wz + xyz' + x'yz$.

 

(b) Series-parallel realization of T .

 


(c) Minimal realization of T .

Sneak path: $z'xx'w$ – OK since it has no effect on the transmission function


35

Synthesis of MOS Networks (Contd.)

 
Example: Design a minimal network to realize $T(w,x,y,z) = \sum(0,3,13,14,15)$



 
(a) Map for $T = wxy + wxz + w'x'y/z' + w'x'yz$.



(b) Series-parallel realization of T .

 

 (c) An alternative series-parallel realization of T .



(d) A minimum realization of T .

36