

## Binary Decision Diagrams

### Assignments

1. For each the following functions, carry out the following for two different orderings of the input variables:
  - Use Shannon decomposition theorem to systematically reduce the given function into sub-functions, and hence create the binary decision diagram (BDD).
  - Apply the reduction rules and create the ROBDD from the BDD.
  - From the ROBDD, arrive at a circuit realization of the function using 2-to-1 multiplexers.
  - (i)  $F(x_1, x_2, x_3) = x_1'x_2 + x_2'x_3$
  - (ii)  $F(a, b, c, d) = (a + b.c)' + b'c'd'$
  - (iii)  $F(a, b, c, d) = a'b'c'd' + a'b'cd + abc'd'$
  - (iv)  $F(a, b, c) = 1$
2. State the reduction rules for converting a BDD to ROBDD with the help of illustrative examples.