
Design for Testability

Basic Concept

- **Design for testability (DFT)**
 - Design techniques that make test generation and test application cost-effective.
- **DFT methods for digital circuits:**
 - Ad-hoc methods
 - Structured methods
 - Scan path
 - Level sensitive scan design
 - Random access scan
 -

Ad-Hoc DFT Methods

- **Good design practices learned through experience are used as guidelines:**
 - **Don't-s and Do-s**
 - **Avoid asynchronous (unclocked) feedback.**
 - **Avoid delay dependant logic.**
 - **Avoid parallel drivers.**
 - **Avoid monostables and self-resetting logic.**
 - **Avoid gated clocks.**
 - **Avoid redundant gates.**

-
- **Avoid high fanin fanout combinations.**
 - **Make flip-flops initializable.**
 - **Separate digital and analog circuits.**
 - **Provide test control for difficult-to-control signals.**


Ad-hoc Methods :: Drawbacks

- **Experts and tools are not always available.**
- **Test generation is often manual, and so high fault coverage is not guaranteed.**
- **Design iterations may be required.**
- **Difficult to automate.**

Structured Methods

- **Helps to provide good controllability and observability of internal state variables for testing.**
 - **Converts the sequential test generation problem into a combinational one.**
- **Major approaches:**
 - **Scan path**
 - **LSSD**
 - **Random access scan**
 - **Variations to above**

A Sequential Circuit

 

Scan Path Design

- **Basic Problem**
 - Test generation for sequential circuits is difficult.
- **Objective**
 - Make all the flip-flops directly controllable and observable.
- **What do we gain?**
 - Combinational circuit test generation can be used.
 - A few additional tests to test the flip-flops (shift register).

Scan Design (contd.)


- **Pre-specified design rules.**
- **Test structure added to the verified design.**
 - Add one (or more) *test control* (TC) primary input.
 - Replace flip-flops by *scan flip-flops*.
 - Connect scan flip-flops to form one or more *shift registers* in test mode.
 - Add SCANIN and SCANOUT pins to shift register.
- **Add *shift register test* and convert ATPG tests into *scan sequences* for use in manufacturing test.**

Scan Design Rules


- **Use only clocked D-type master-slave flip-flops for all state variables.**
- **At least one PI pin must be available for test; more pins, if available, can be used.**
- **All clocks must be controlled from PIs.**
 - **Necessary for flip-flops to work in scan registers.**
- **Clocks must not feed data inputs of flip-flops.**
 - **May lead to race condition.**

Correcting a Rule Violation

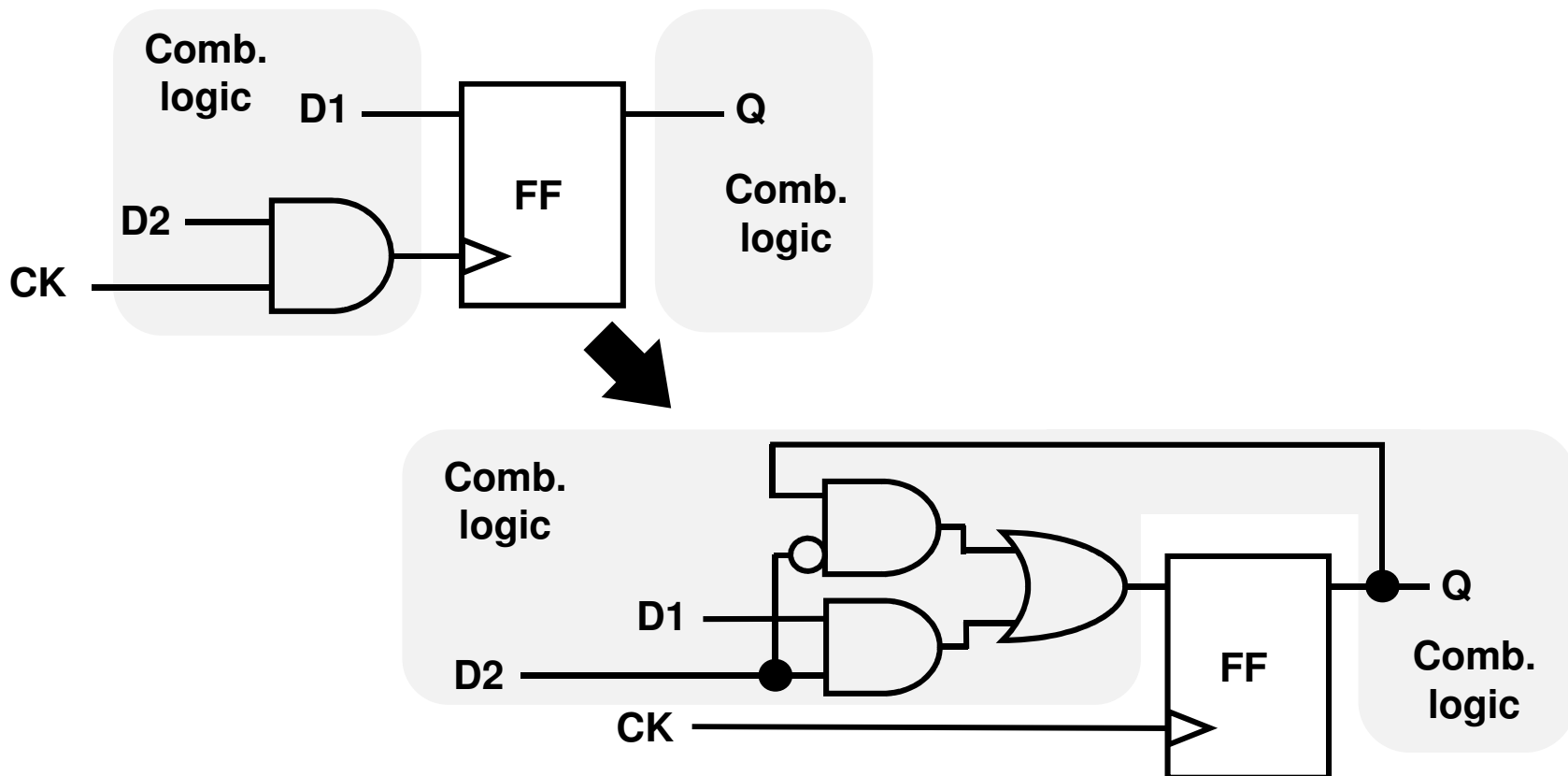
- All clocks must be controlled from PIs.



Scan Flip-Flop (master-slave)

 


Adding Scan Structure

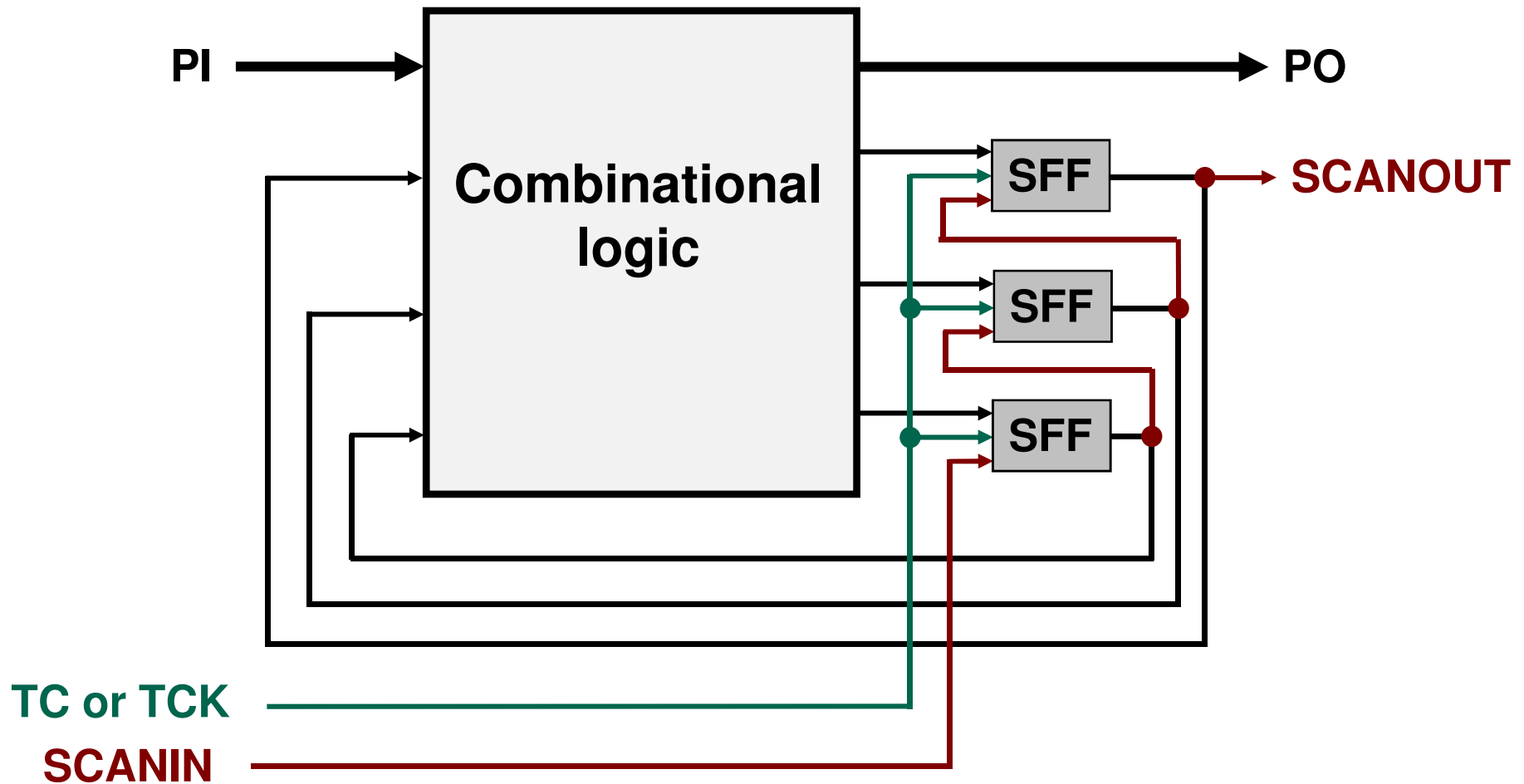


-
- **Application of the test vectors:**

PI	Present State	PO	Next State
I1	S1	O1	N1
I2	S2	O2	N2
I3	S3	O3	N3
...

Combinational Test Vectors

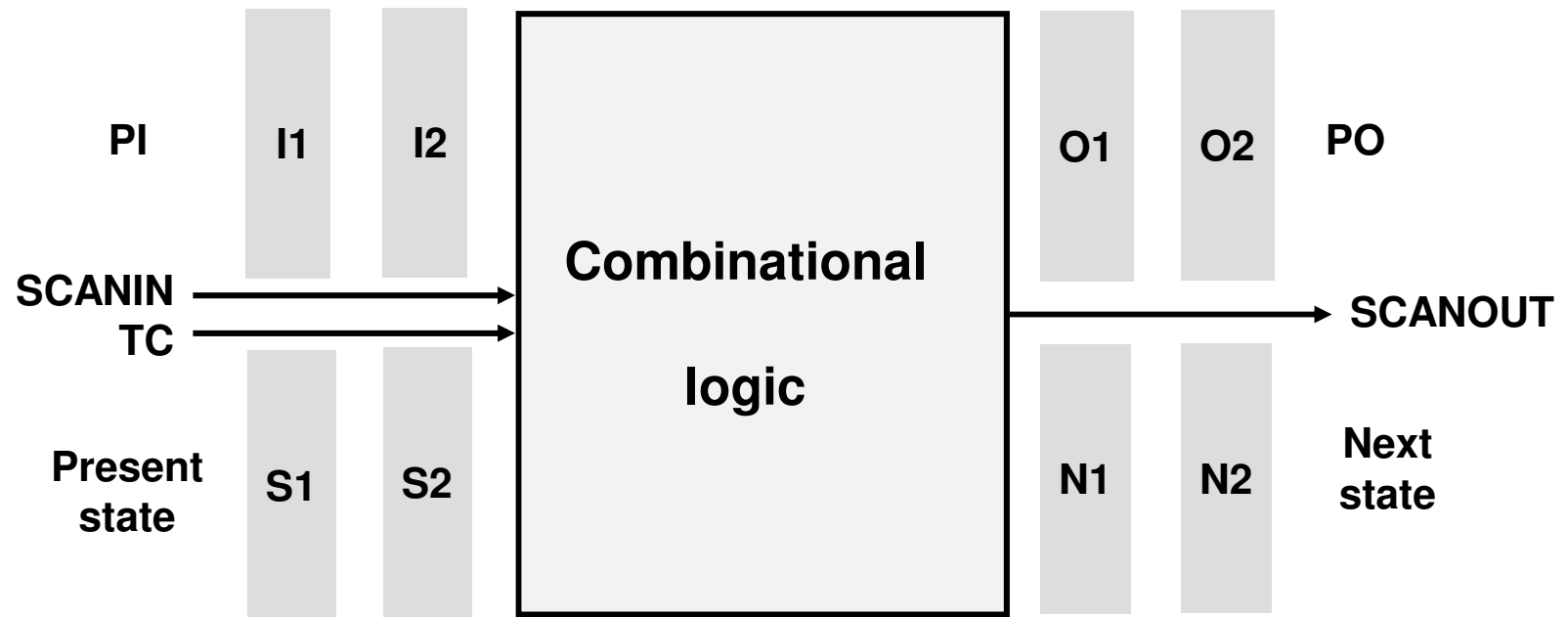

Combinational Test Vectors

 

-
- **Scan sequence length:**

$$(n_s + 1) n_c + n_s \text{ clock periods}$$

where n_c : number of combinational test vectors

n_s : number of scan flip-flops

An example: the I/O specifications

3 inputs, 2 outputs, and 3 state variables

PI	Present State	PO	Next State
0 1 0	1 0 0	0 1	1 0 1
0 1 1	0 1 0	1 1	0 0 1
1 0 1	1 0 0	1 0	1 1 1
0 0 1	1 0 1	0 1	0 1 0

contd. : corresponding scan sequence

Clock	PI	SCANIN	TC	PO	SCANOUT
1	xxx	1	0	xx	x
2	xxx	0	0	xx	x
3	xxx	0	0	xx	x
4	010	x	1	01	x
5	xxx	0	0	xx	1
6	xxx	1	0	xx	0
7	xxx	0	0	xx	1
8	011	x	1	11	x

Scan Testing Time

- **Scan register has to be tested prior to the application of scan test sequences.**
 - A shift sequence 00110011... of length n_s+4 .
 - Produces all possible transitions in all flip-flops.
- **Total scan test length:**


$$(n_s + 1) n_c + n_s + (n_s + 4)$$

n_s : number of scan flip-flops

n_c : number of combinational test vectors

$n_s=2000, n_c=500 \rightarrow \text{Test length} = 10^6$

A Typical Module With Scan Chains

 

Multiple Scan Paths

- Scan flip-flops can be distributed among any number of shift registers, each having a separate *SCANIN* and *SCANOUT* pin.
 - PI and PO pins can be shared with *SCANIN* and *SCANOUT* pins respectively.
- Test sequence length is determined by the longest scan shift register.
- Just one test control (TC) pin is essential.

Other Issues

- **Multiple scan paths can reduce test application time.**
- **Scan overhead:**
 - **One additional pin (TC)**
 - **Other pins can be multiplexed with functional input and output pins.**
 - **Area overhead**
 - **Replacing flip-flops by scan flip-flops.**
 - **Performance overhead**
 - **Additional MUX-es in critical path.**
 - **Increase in fanout for the flip-flops.**

Scan Overheads

- **IO pins:**
 - One pin necessary.

- **Area overhead:**

$$\text{Gate overhead} = [4 n_s / (n_g + 10n_s)] \times 100\%$$

where n_g = number of *gates in combinational logic*

n_s = number of *flip-flops*

- **Example:**


- $n_g = 100\text{k gates}$, $n_s = 2\text{k flip-flops}$, overhead = 6.7%.

- **More accurate estimate must consider scan wiring and layout area.**

-
- **Performance overhead:**
 - **Multiplexer delay added in combinational path; approx. two gate-delays.**
 - **Flip-flop output loading due to one additional fanout; approx. 5-6%.**

Hierarchical Scan

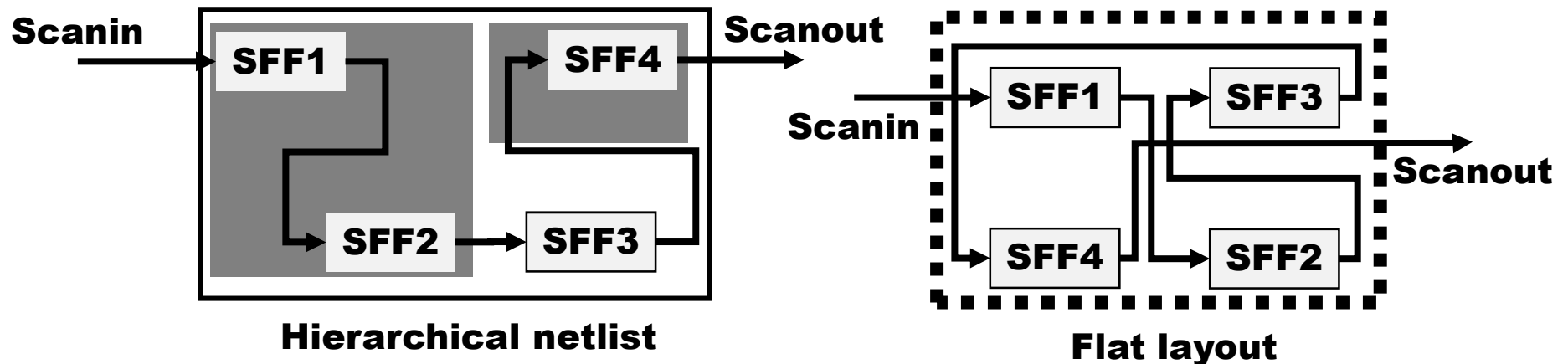- Scan flip-flops are chained within subnetworks before chaining subnetworks.
- Advantages:
 - Automatic scan insertion in netlist
 - Circuit hierarchy preserved – helps in debugging and design changes
- Disadvantage: Non-optimum chip layout.



ATPG Example: S5378

	Original	Full-scan
Number of combinational gates	2,781	2,781
Number of non-scan flip-flops (10 gates each)	179	0
Number of scan flip-flops (14 gates each)	0	179
Gate overhead	0.0%	15.66%
Number of faults	4,603	4,603
PI/PO for ATPG	35/49	214/228
Fault coverage	70.0%	99.1%
Fault efficiency	70.9%	100.0%
CPU time on SUN Ultra II, 200MHz processor	5,533 s	5 s
Number of ATPG vectors	414	585
Scan sequence length	414	105,662

Summary

- **Scan is the most popular DFT technique:**
 - Rule-based design
 - Automated DFT hardware insertion
 - Combinational ATPG
- **Advantages:**
 - Design automation
 - High fault coverage; helpful in diagnosis
 - Hierarchical – scan-testable modules are easily combined into large scan-testable systems
 - Moderate area (~10%) and speed (~5%) overheads



-
- **Disadvantages:**
 - **Large test data volume and long test time**
 - **Basically a slow speed (DC) test**

Level Sensitive Scan Design

- **Similar to scan path in concept; uses level sensitive latches.**
- **Main issues:**
 - **Absence of races and hazards.**
 - **Insensitive to rise time, fall time, delay, etc.**
 - **Lower hardware complexity as compared to scan path design.**
 - **More complex design rules.**

LSSD

Polarity-Hold Latch:

  


C	D	+L
0	0	L
0	1	L
1	0	0
1	1	1

- The correct change of the latch output (L) is not dependent on the rise/fall time of C, but only on C being '1' for a period of time \geq data propagation and stabilization time.

LSSD

 Polarity-Hold Shift-Register Latch (SRL):




- **Normal mode:** $A = B = 0, C = 0 \rightarrow 1$.
- **SR (test) mode:** $C = 0, AB = 10 \rightarrow 01$ to shift SI through L_1 and L_2 .


LSSD

- **Polarity-Hold, hazard-free, and level-sensitive.**
- **To be race-free, clocks C & B as well as A & B must be non-overlapping.**
- **Avoids performance degradation introduced by the MUX in shift-register modification.**


Double-Latch LSSD

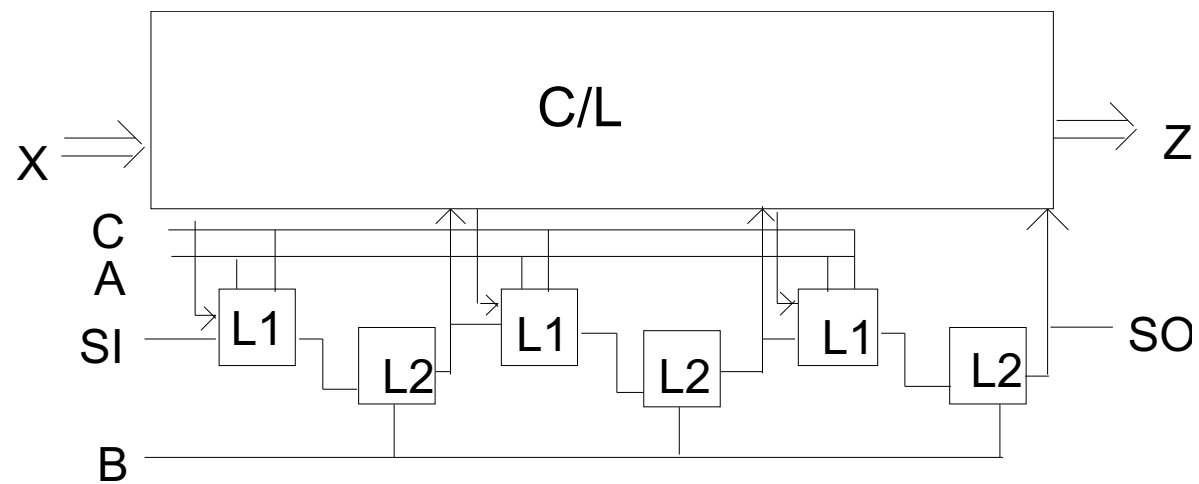


Single-Latch LSSD

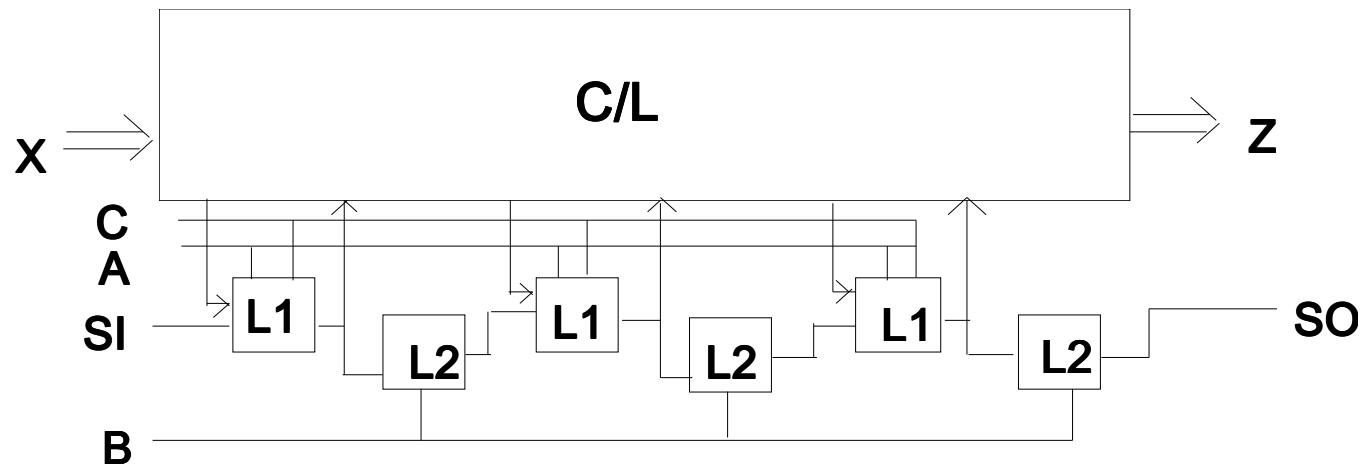

Single-Latch LSSD With Conventional SRLs

 


SRL Using Two-Port L_2^*

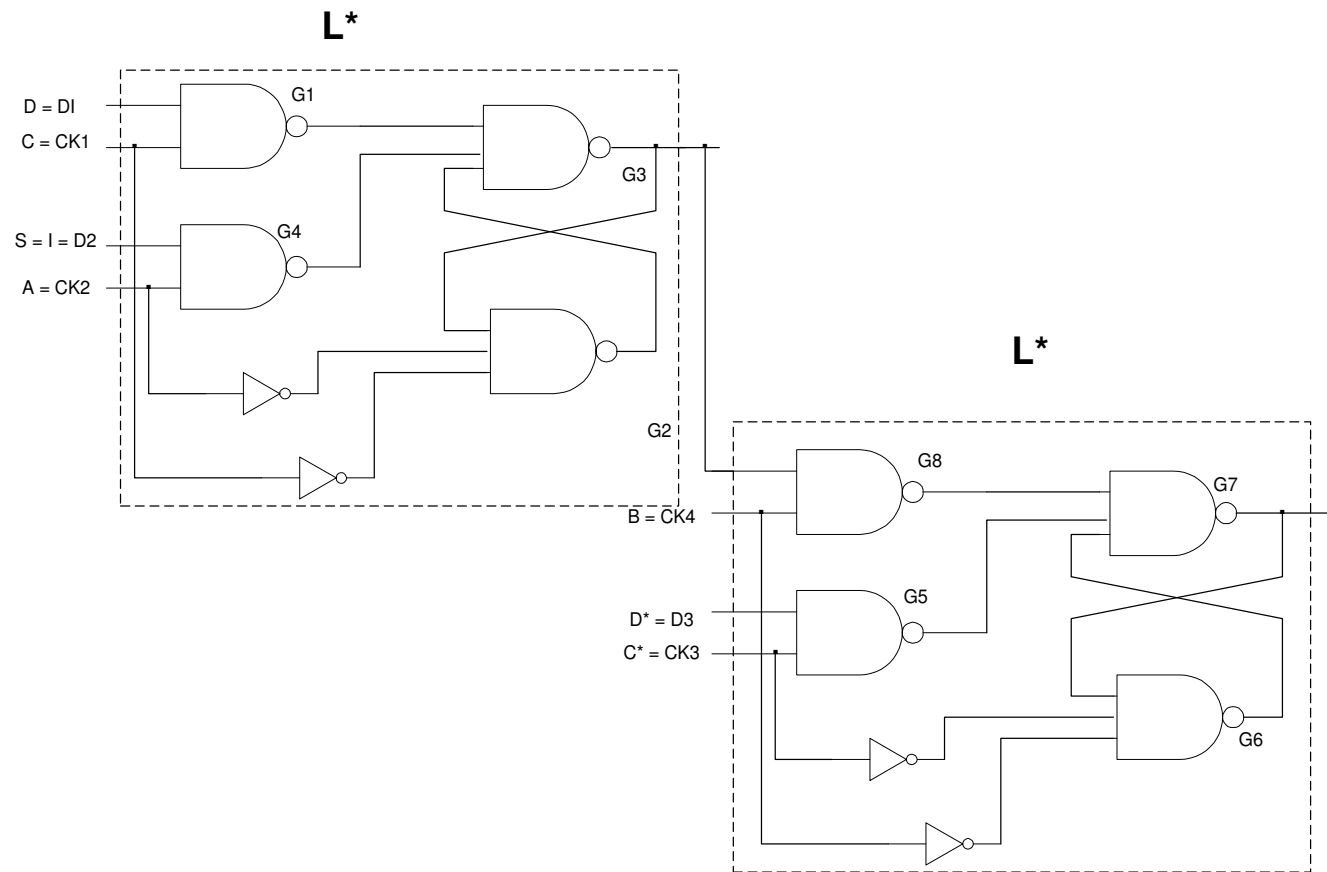


(a) Gate model

SRL Using Two-Port L_2^*

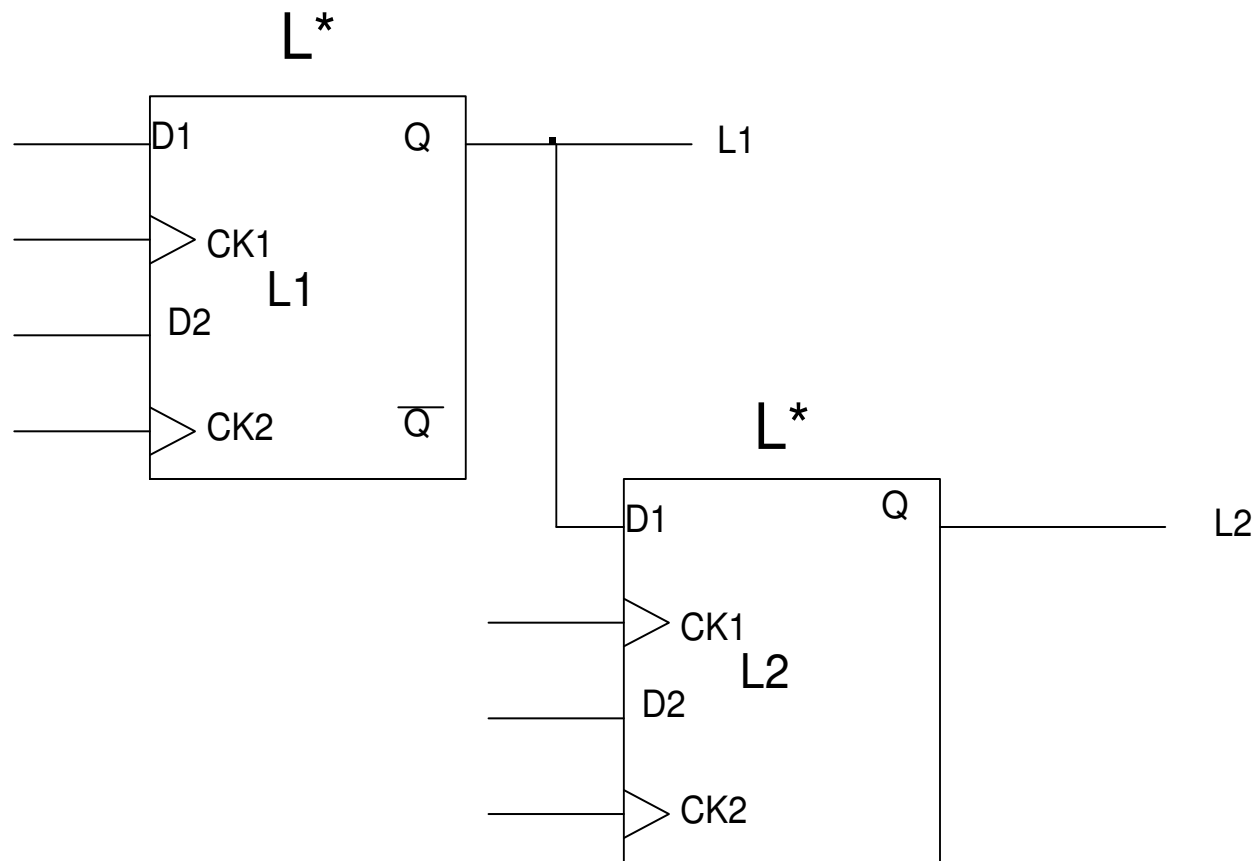

(b) Symbol

Single-Latch LSSD With L_2^* Latches

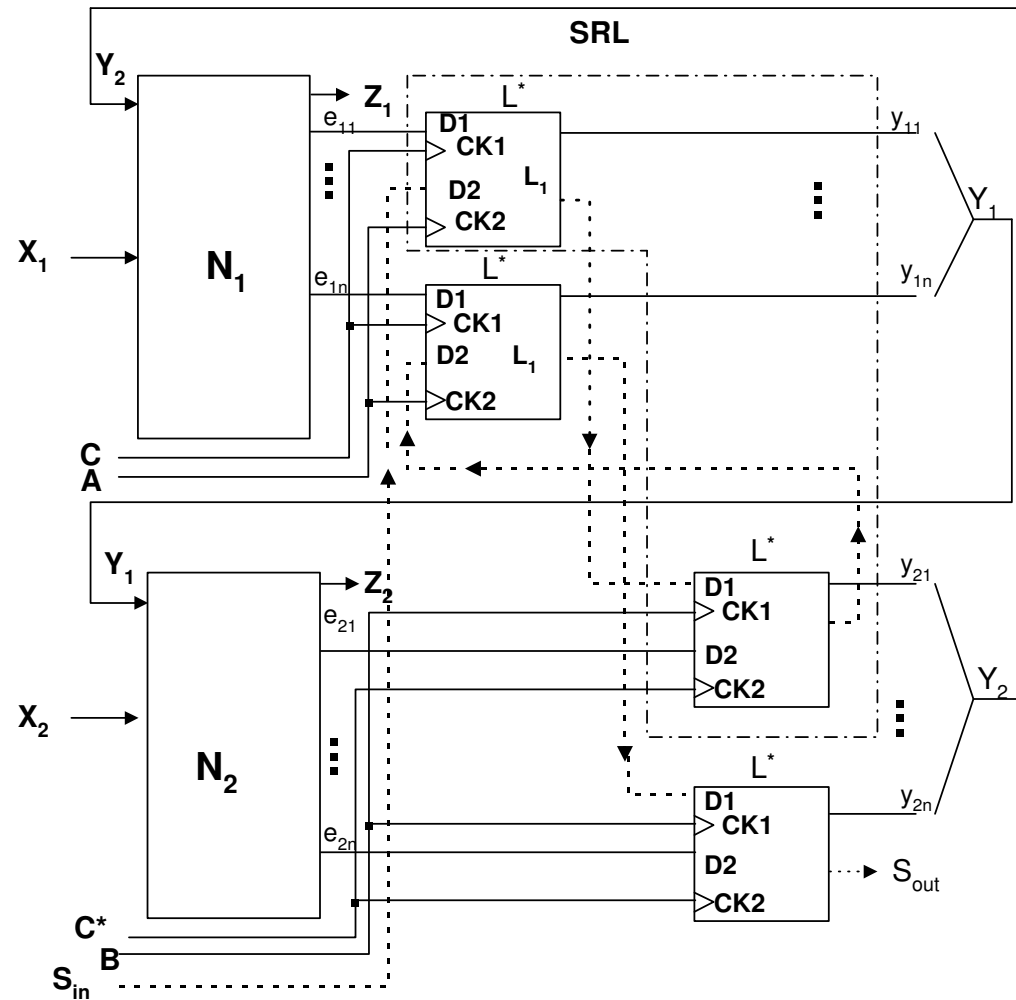

LSSD Design Rules

- 1. Internal storage elements must be polarity-hold latches.**
- 2. Latches can be controlled by 2 or more non-overlapping clocks that satisfy:**
 - A latch X may feed the data port of another latch Y iff the clock that sets the data into Y does not clock X.**
 - A latch X may gate a clock C to produce a gated clock C_g , which drives another latch Y iff C_g , or any other clock C_{1g} , produced from C_g , does not clock X.**

LSSD Design Rules (contd.)

- 3. There must exist a set of clock primary inputs from which the clock inputs to all SRLs are controlled either through (1) single-clock distribution tree, or (2) logic that is gated by SRLs and/or non-clock primary inputs. In addition, the following conditions must hold:**
 - All clock inputs to SRLs must be OFF when clock PIs are OFF.**
 - Any SRL clock input must be controlled from one or more clock PIs.**
 - No clock can be ANDed with either the true or the complement of another clock.**

LSSD Design Rules (contd.)

- 4. Clock PIs cannot feed the data inputs to latches, either directly or through combinational logic.**
- 5. Every system latch must be part of an SRL; each SRL must be part of some scan chain.**
- 6. A scan state exists under the following conditions:**
 - Each SRL or scan-out PO is a function of only the preceding SRL or scan-in PI in its scan chain during the scan operation.**
 - All clocks except the shift clocks are disabled at the SRL inputs.**

LSSD Design Rules (contd.)

- 7. Any shift clock to an SRL can be turned ON or OFF by changing the corresponding clock PI.**
 - A network that satisfies rules 1-4 is level-sensitive.**
 - Race-free operation is guaranteed by rules 2(1) & 4.**
 - Rule 3 allows a tester to turn off system clocks and use the shift clocks to force data into and out of the scan chain.**
 - Rules 5 & 6 are used to support scan.**

Advantages With LSSD

- **Correct operation independent of AC characteristics.**
- **Reducing FSM to C/L as far as testing is concerned.**
- **Eliminating hazards & races; simplifying test generation and fault simulation.**

Problems With LSSD

- **Design rules imposed on designers --- no freedom to vary from the overall schemes, and higher design and hardware costs (4-20% more h/w & 4 extra pins).**
- **No asynchronous designs.**
- **Sequential routing of latches can introduce irregular structures.**
- **Faults changing combinational function to sequential may cause trouble, e.g., bridging, CMOS stuck-open.**
- **Slow test application; normal-speed testing is impossible.**
- **Not good for memory intensive designs.**