
Verilog HDL

Testing & Verification

Dept. of Computer Science & Engg, IIT Kharagpur



Pallab Dasgupta

Professor, Dept. of Computer Science & Engg.,
Professor-in-charge, AVLSI Design Lab,
Indian Institute of Technology Kharagpur

Agenda

- **Structural Hardware Models**
- **4-Valued Logic**
- **Delay**
- **Instantiation**
- **Wiring**
- **Test Benches**
- **Behavioral Models**
- **Concurrency**
- **Summary**

Source: The Verilog Hardware Description Language,
By Thomas and Moorby, Kluwer Academic Publishers


Representation: Structural Models

□ Structural models

- Are built from gate primitives and/or other modules
- They describe the circuit using logic gates — much as you would see in an implementation of a circuit.

□ Identify:

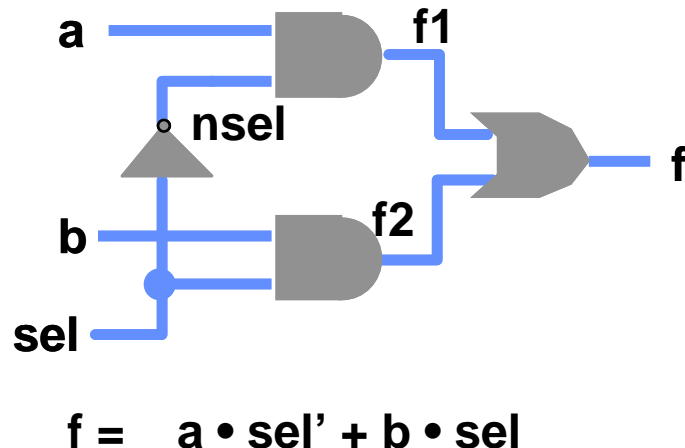- Gate instances, wire names, delay from *a* or *b* to *f*.
- This is a multiplexor — it selects one of *n* inputs (2 here) and passes it on to the output



```
module MUX (f, a, b, sel);
output      f;
input       a, b, sel;

    and #5  g1 (f1, a, nsel),
           g2 (f2, b, sel);
    or  #5  g3 (f, f1, f2);
    not          g4 (n sel, sel);
endmodule
```

Representation: Gate-Level Models

❑ Need to model the gate's:

- Function
- Delay

❑ Function

- Generally, HDLs have built-in gate-level primitives
 - Verilog has NAND, NOR, AND, OR, XOR, XNOR, BUF, NOT, and some others
- The gates operate on input values producing an output value
 - Typical Verilog gate instantiation is:

optional
and #delay instance-name (out, in1, in2, in3, ...);

“many”

and #5 g1 (f1, a, nsel);

a comma here let's you list other instance names and their port lists.

Four-Valued Logic

❑ Verilog Logic Values

- The underlying data representation allows for any bit to have one of four values
- 1, 0, x (unknown), z (high impedance)
- x — one of: 1, 0, z, or in the state of change
- z — the high impedance output of a tri-state gate.

Four-Valued Logic

- ❑ **What basis do these have in reality?**
 - 0, 1 ... no question
 - z ... A *tri-state* gate drives either a zero or one on its output ...and if it's not doing that, its output is high impedance (z). Tri-state gates are real devices and z is a *real* electrical affect.
 - x ... not a real value. There is no *real* gate that drives an x on to a wire. x is used as a *debugging* aid. x means the simulator can't determine the answer and so maybe you should worry!
All values in a simulation start as x.

- ❑ **BTW ...**
 - Verilog keeps track of more values than these in some situations.

Four-Valued Logic

❑ Logic with multi-level logic values

- Logic with these four values make sense
 - Nand anything with a 0, and you get a 1. This includes having an x or z on the other input. That's the nature of the nand gate
 - Nand two x's and you get an x — makes sense!
- Note: z treated as an x on input. Their rows and columns are the same
- If you forget to connect an input ... it will be seen as an z.
- At the start of simulation, *everything* is an x.


		Input B			
		Nand	0	1	x
Input A	0	1	1	1	1
	1	1	0	x	x
	x	1	x	x	x
	z	1	x	x	x



A 4-valued truth table for a Nand gate with two inputs

Delay



- **Transport delay — input to output delay**
 - “nand #35 (f1, a, b, c);” #35 is the transport delay
- **What if the input changes during that time?**
 - i.e., how wide must an input spike be to affect the output?
 - Think of the gate as having inertia. — The input change must be present long enough to get the output to change. (That “long enough” time is called *inertial* delay)
 - in Verilog, this time is equal to the transport delay

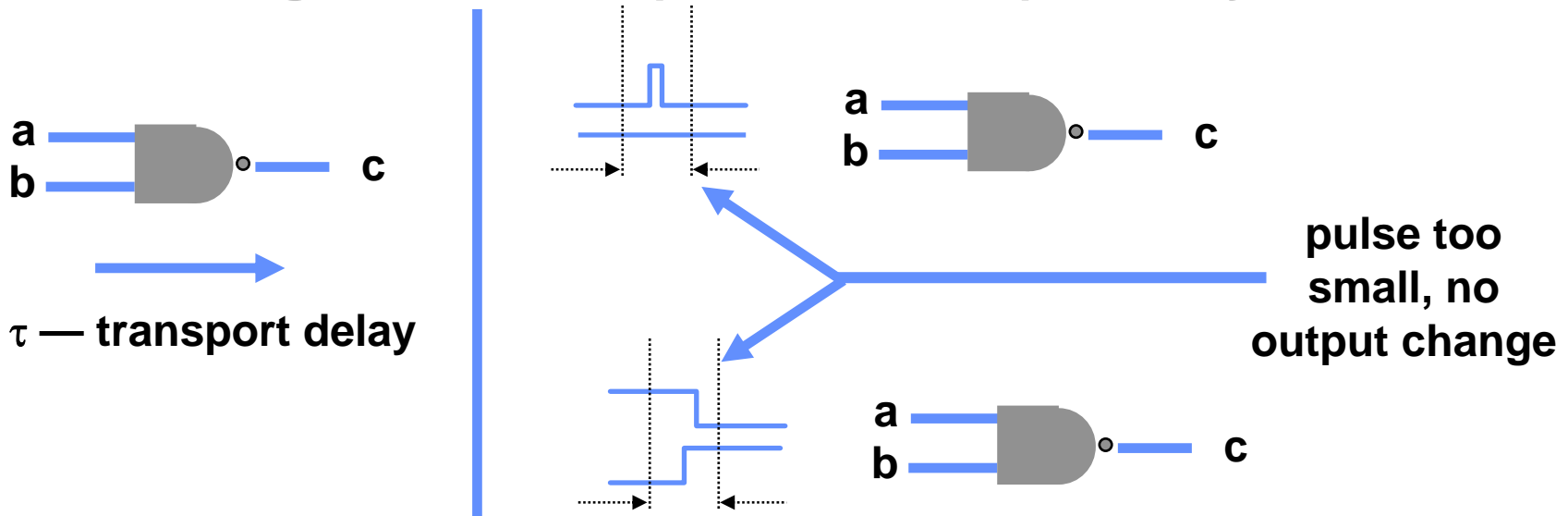

Let's Build a Wider 2-bit MUX

□ Build a 2-bit 2:1 MUX

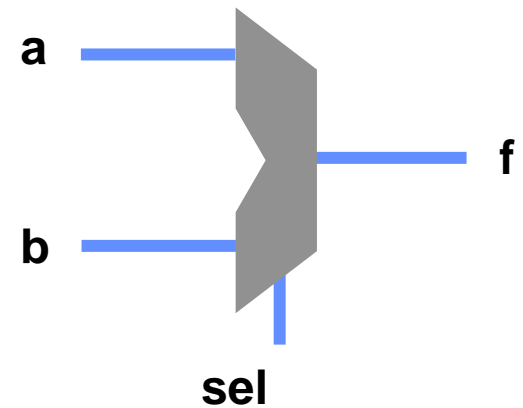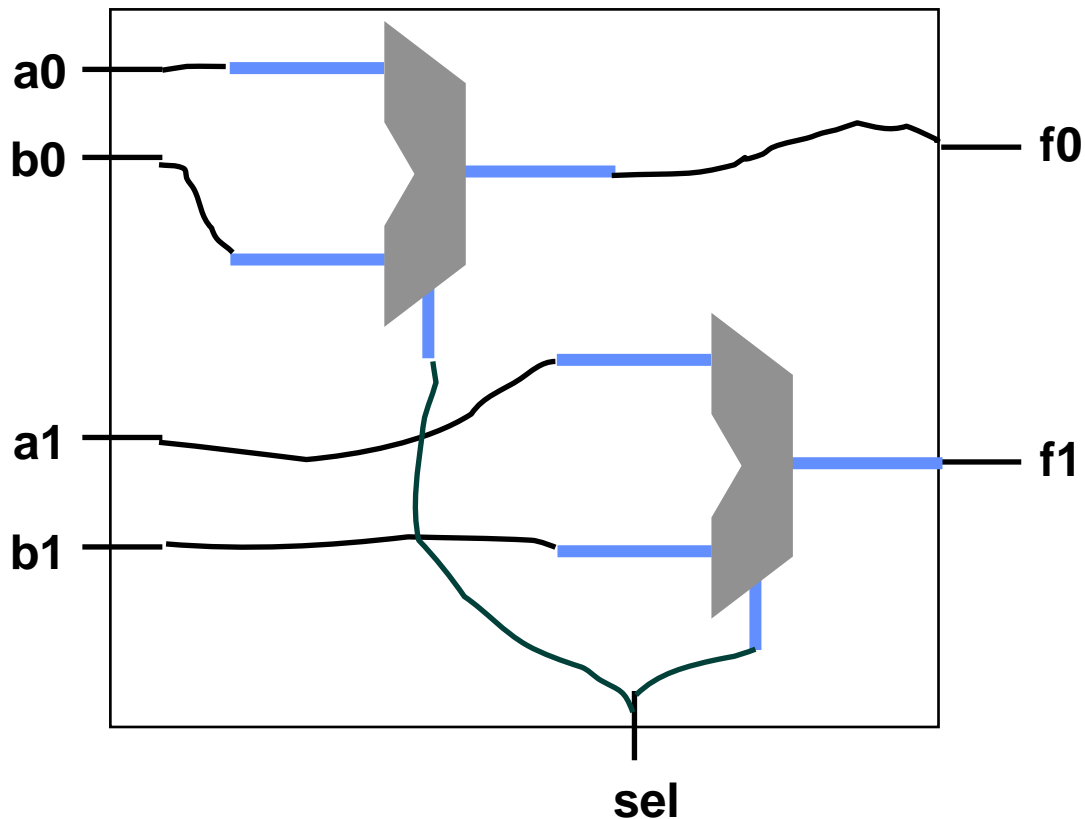- OK, let's put two 1-bit 2:1 MUXes in the same module with a common select line
- What would it look like?



Reuse!

❑ Reuse of smaller objects

- Can we use the MUX module that we already designed?
- A big idea — *instantiation*
- Modules and primitive gates can be *instantiated* — copied — to many sites in a design
- Previously, two ANDs, one OR, and a NOT gate were instantiated into module MUX
- Now we instantiate two copies of module MUX into module wideMux

```
module wideMux (f1, f0, a1, a0, b1, b0, sel);  
  input  a1, a0, b1, b0, sel;  
  output f1, f0;  
  
  MUX   bit1 (f1, a1, b1, sel),  
        bit0 (f0, a0, b0, sel);  
endmodule
```

Instantiate two MUX modules, name them, and specify connections (the order is important).

Instantiation — Copies

- ❑ **Modules and gate primitives are *instantiated* == copied**
 - **Note the word “copies”**
 - **The copies (also called *instances*) share the module (or primitive) definition**
 - **If we ever change a module definition, the copies will all change too**
 - **However, the internal entities (gate names, internal port names, and other things to come) are all private, separate copies**

Instantiation — Copies

- ❑ **Modules and gate primitives are *instantiated* == copied**
 - **Don't think of module instantiations as subroutines that are called**
 - **They are copies — there are 2 MUX modules in wideMux with a total of:**

4 AND gates,

2 OR gates,

2 NOT gates

Why Is This Cool?

❑ In Verilog

- “Primitive” gates are predefined (NAND, NOR, ...)
- Other modules are built by instantiating these gates
- Other modules are built by instantiating other modules, ...

❑ The design *hierarchy* of modules is built using instantiation

- Bigger modules of useful functionality are defined
- You can then design with these bigger modules
 - You can reuse modules that you’ve already built and tested
 - You can hide the detail — why show a bunch of gates and their interconnection when you know it’s a mux!

❑ Instantiation & hierarchy control complexity.

- No one designs 1M+ random gates — they use hierarchy.
- What are the software analogies?

How to Wire Modules Together

- ❑ Real designs have many modules and gates

```
module putTogether ();  
wire w1, w2, w3, w4;  
  
    bbb    lucy    (w1, w2, w3, w4);  
    aaa    ricky  (w3, w2, w1);  
    ...  
endmodule
```

what happens when
out1 is set to 1?

```
module bbb (i1, i2, o1, clk);  
input      i1, i2, clk;  
output     o1;  
  
    xor (o1, i2, ...);  
    ...  
endmodule
```

```
module aaa (in1, out1, out2);  
input      in1;  
output     out1, out2;  
  
    ...  
  
    nand #2 (out1, in1, b);  
    nand #6 (out2, in1, b);  
    ...  
endmodule
```

Each module has its own namespace. Wires connect elements of namespaces.

Implicit Wires

- How come there were no wires declared in some of these modules?
 - **Gate** instantiations implicitly declare wires for their outputs.
 - All **other** connections must be **explicitly declared as wires** — for instance, connections between module ports
 - Output and input declarations are wires

```
module putTogether ();  
    wire    w1, w2, w3, w4;  
  
    mux    inst1 (w1, w2, w3, w4);  
    aaa    duh (w3, w2, w1);  
    ...
```

wires explicitly
declared

```
module mux (f, a, b, sel);  
    output    f;  
    input     a, b, sel;  
  
    and #5    g1 (f1, a, nsel),  
            g2 (f2, b, sel);  
  
    or  #5    g3 (f, f1, f2);  
    not      g4 (nsel, sel);  
endmodule
```

wires implicitly
declared (f1, f2, nsel)

How to Build and Test a Module

- ❑ **Construct a “test bench” for your design**
 - Develop your hierarchical system within a module that has input and output ports (called “**design**” here)
 - Develop a separate module to generate tests for the module (“**test**”)
 - Connect these together within another module (“**testbench**”)

```
module testbench ();  
    wire    l, m, n;  
  
    design  d (l, m, n);  
    test    t (l, m);  
  
    initial begin  
        //monitor and display  
        ...  
    end
```


```
module design (a, b, c);  
    input  a, b;  
    output c;  
    ...  
end
```

```
module test (q, r);  
    output q, r;  
  
    initial begin  
        //drive the outputs with signals  
        ...  
    end
```


Another View of This

- 3 chunks of Verilog, one for each of:

 TESTBENCH is the final piece of hardware which connects DESIGN with TEST so the inputs generated go to the thing you want to test...



An Example

Module testAdd generated inputs for module halfAdd and displayed changes. Module halfAdd was the *design*

```
module tBench;
    wire    su, co, a, b;

    halfAdd    ad (su, co, a, b);
    testAdd    tb (a, b, su, co);
endmodule
```

```
module halfAdd (sum, cOut, a, b);
    output    sum, cOut;
    input     a, b;

    xor #2    (sum, a, b);
    and #2    (cOut, a, b);
endmodule
```

```
module testAdd (a, b, sum, cOut);
    input    sum, cOut;
    output   a, b;
    reg     a, b;

    initial begin
        $monitor ($time,,
            "a=%b, b=%b, sum=%b, cOut=%b",
            a, b, sum, cOut);
        a = 0; b = 0;
        #10 b = 1;
        #10 a = 1;
        #10 b = 0;
        #10 $finish;
    end
endmodule
```

The Test Module

❑ It's the test generator

❑ \$monitor

- prints its string when executed.
- after that, the string is printed when one of the listed values changes.
- only one monitor can be active at any time
- prints at end of current simulation time

❑ Function of this tester

- at time zero, print values and set a=b=0
- after 10 time units, set b=1
- after another 10, set a=1
- after another 10 set b=0
- then another 10 and finish

```
module testAdd(a, b, sum, cOut);
    input  sum, cOut;
    output a, b;
    reg    a, b;

    initial begin
        $monitor ($time,,
            "a=%b, b=%b, sum=%b,
            cOut=%b",
            a, b, sum, cOut);
        a = 0; b = 0;
        #10 b = 1;
        #10 a = 1;
        #10 b = 0;
        #10 $finish;
    end
endmodule
```

Another Version of a Test Module

❑ Multi-bit “thingies”

- test is a two-bit register and output
- It acts as a two-bit number (counts 00-01-10-11-00...)
- Module tBench needs to connect it correctly — mod halfAdd has 1-bit ports.

```
module tBench;  
  wire  su, co;  
  wire [1:0] t;  
  
  halfAdd  ad (su, co, t[1], t[0]);  
  testAdd  tb (t, su, co);  
endmodule
```

```
module testAdd (test, sum, cOut);  
  input          sum, cOut;  
  output [1:0] test;  
  reg  [1:0] test;  
  
  initial begin  
    $monitor ($time,,  
              "test=%b, sum=%b, cOut=%b",  
              test, sum, cOut);  
    test = 0;  
    #10 test = test + 1;  
    #10 test = test + 1;  
    #10 test = test + 1;  
    #10 $finish;  
  end  
endmodule
```

Connects bit 0 or wire t to this port (b of the module halfAdder)

Another Version of testAdd

❑ Other procedural statements

- You can use “for”, “while”, “if-then-else” and others here.
- This makes it easier to write if you have lots of input bits.

```
module tBench;  
  wire su, co;  
  wire [1:0] t;  
  
  halfAdd ad (su, co, t[1], t[0]);  
  testAdd tb (t, su, co);  
endmodule
```

```
module testAdd (test, sum, cOut);  
  input          sum, cOut;  
  output [1:0]   test;  
  reg   [1:0]   test;  
  
  initial begin  
    $monitor ($time,,  
      "test=%b, sum=%b, cOut=%b",  
      test, sum, cOut);  
    for (test = 0; test < 3; test = test + 1)  
      #10;  
    #10 $finish;  
  end  
endmodule
```

hmm... “<3” ... ?

Structural Vs. Behavioral Models

❑ Structural model

- Just specifies primitive gates and wires
- i.e., the structure of a logical netlist
- You basically know how to do this now.

❑ Behavioral model

- More like a procedure in a programming language
- Still specify a module in Verilog with inputs and outputs...
- ...but inside the module you write code to tell what you want to have happen, NOT what gates to connect to make it happen
- i.e., you specify the behavior you want, not the structure to do it

❑ Why use behavioral models

- For testbench modules to test structural designs
- For high-level specs to drive logic synthesis tools

How Do Behavioral Models Fit In?

□ How do they work with the event list and scheduler?

- Initial (and always) begin executing at time 0 in arbitrary order
- They execute until they come to a “#delay” operator
- They then suspend, putting themselves in the event list 10 time units in the future (for the case at the right)
- At 10 time units in the future, they resume executing where they left off.

□ Some details omitted

- ...more to come

```
module testAdd (a, b, sum, cOut);  
    input    sum, cOut;  
    output  a, b;  
    reg     a, b;  
  
    initial begin  
        $monitor ($time,,  
            “a=%b, b=%b,  
            sum=%b, cOut=%b”,  
            a, b, sum, cOut);  
        a = 0; b = 0;  
        #10 b = 1;  
        #10 a = 1;  
        #10 b = 0;  
        #10 $finish;  
  
    end  
endmodule
```

Concurrent Activity

Eval g2, g3

- Do these two evaluations happen at the same time?**
 - Yes and No! Yes and No!
- Yes ...**
 - They happen at the same *simulated* (or virtual) time
 - After all, the time when they occur is 27
- No ...**
 - We all know the processor is only doing one thing at any given time
- So, which is done first?**
 - That's undefined. We can't assume anything except that the order is arbitrary.

Concurrent Activity

- ❑ **The point is**
 - In the real implementation, all activity will be concurrent
 - Thus the simulator models the elements of the system as being concurrent in simulated time
 - **The simulator stands on its head trying to do this!**

- ❑ **Thus,**
 - Even though the simulator executes each element of the design one at a time ...
 - ... we'll call it concurrent

Behavioral Verilog HDL codes

```
module module_name(port_names);  
input [port_size] input_port_names;  
output [port_size] output_port_names;  
wire [wire_size] wire_names;  
reg [reg_size] reg_names;
```

```
always @(sensitivity list)
```

```
- - - -
```

```
behavioral statements
```

```
- - - -
```

```
endmodule
```

Multiplexer

```
module mux (f, a, b, sel);  
input [3:0] a, b;  
input sel;  
output [3:0] f;  
reg [3:0] f;  
always @(a or b or sel)  
if (sel)  
    f=b;  
else  
    f=a;  
endmodule
```

Flip-flop Design: *An Example*

```
module DFF(d, q, qbar, clk, reset);  
input d, clk, reset;  
output q, qbar;  
reg q, qbar;  
    always @(posedge clk or posedge reset)  
    begin  
        if (sel)  
            begin q = 1'b0; qbar = 1'b1; end  
        else  
            begin q = d; qbar = ~d; end  
        end  
endmodule
```

Behavioral Statements

- ❑ **Continuous assignment statements**
 - using *assign*

- ❑ **Procedural assignment statements**
 - Blocking assignment (using =)
 - Non blocking assignment (using <=)

Blocks Statements

❑ Sequential Block Statements:

- Sequential block is a group of statements between a *begin* and an *end*.
- A sequential block, in an *always* statement executes repeatedly
- Inside an *initial* statement, it operates only once

❑ Parallel Block Statements:

- Statements are enclosed within

fork

join

Block statements: *Examples*

```
always @(a or b or c);  
begin  
#5 d = a+b;  
#10 e = a-c;  
#15 f = b+c;  
end
```

```
initial  
begin  
#5 d = a+b;  
#10 e = a-c;  
#15 f = b+c;  
end
```

```
always @(a or b or c);  
fork  
#5 d = a+b;  
#10 e = a-c;  
#15 f = b+c;  
join
```

Examples

❑ Blocking:

always @(A1 or B1 or C1 or M1)

begin

M1 = #3 (A1 & B1);

Y1 = #1 (M1 | C1);

end

❑ Statement executed at time t causing M1 to be assigned at t+3

❑ Statement executed at time t+3 causing Y1 to be assigned at time t+4

❑ Non-blocking:

always @(A2 or B2 or C2 or M2)

begin

M2 <= #3 (A2 & B2);

Y2 <= #1 (M1 | C1);

end


❑ Statement executed at time t causing M2 to be assigned at t+3

❑ Statement executed at time t causing Y2 to be assigned at time t+1. Uses old values.

 Example: *Implementation*

❑ Blocking Assignment

```
module BA(clk, a, b, c)
input clk, a, b;
output c;
reg b, c;
always @(posedge clk)
begin
    b=a; c=b;
end
endmodule
```



Example: *Implementation*

❑ Non Blocking Assignment

```
module NBA(clk, a, b, c)
```

```
input clk, a, b;
```

```
output c;
```

```
reg b, c;
```


```
always @(posedge clk)
```

```
begin
```

```
    b<=a; c<=b;
```

```
end
```

```
endmodule
```

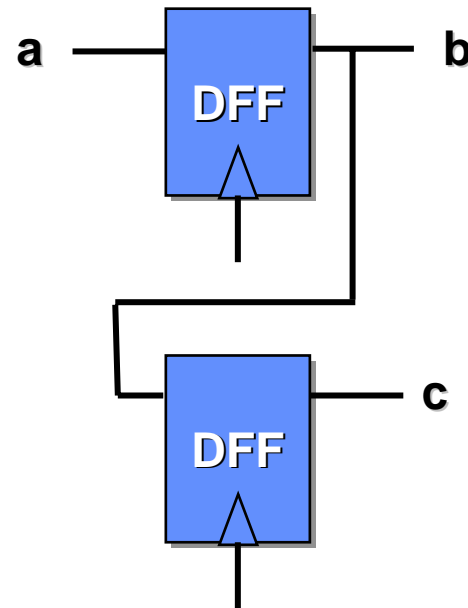

Design using Functions and Tasks

❑ Function

```
module m_name( port_declarations)
  ---
begin
  ---
  ret_val = func_name(arguments);
end

function func_name;
  input declaration
  variable declaration
  begin
    <statements>
  end
endfunction

endmodule
```

❑ Task


```
module m_name( port_declarations)
  ---
begin
  ---
  task_name(arguments);
end

task task_name;
  input declaration
  output declaration
  variable declaration
  begin
    <statements>
  end
endtask

endmodule
```

FSM Design using Verilog HDL
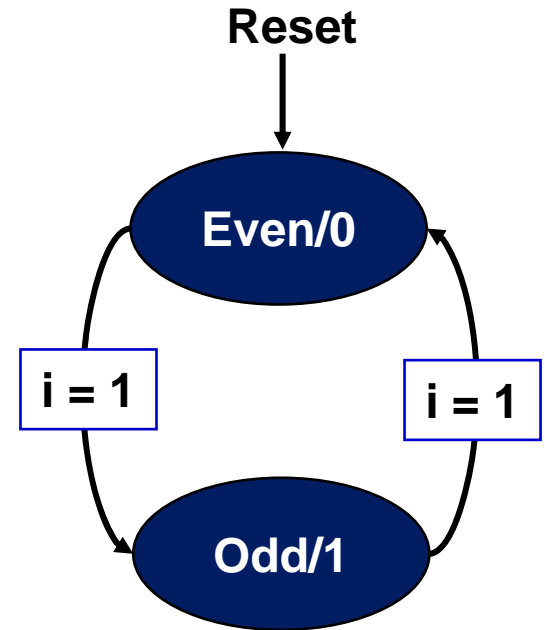
```
module parity (clk, reset, i, o) ;
input clk, reset, i;
output o;
reg st, next_st, o;
parameter st_even = 0, st_odd = 1;
always @ (posedge clk or posedge reset)
begin
    if (reset == 1)
        st <= st_even;
    else
        st <= next_st;
end
/* State transitions */
/* Output computation */
endmodule
```



State Transitions & O/P computations

// State Transitions

always @ (i or st)

begin

if (i==1) begin

if (st == st_even)

next_st = st_odd;

else next_st = st_even;

end

else next_st = st;

end

// Output Computation

always @(st)

begin

if (st == st_even) o=0;

else o=1;

end

