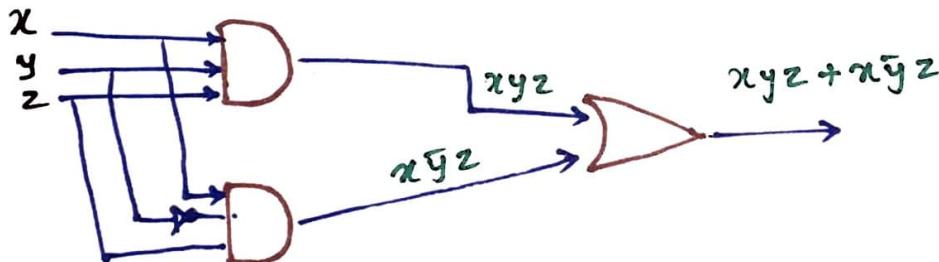


13 Week X: Lecture Notes

Minimization of circuits.

- The efficiency of a combinational circuit depends on the number and arrangements of its gates.
- The process of designing a combinational circuit:
 - Begin with the table specifying the output for each combination of input values.
 - May use the sum-of-product expansion of the circuit and find a set of logic gates.
- The sum-of-product expansion may contain many more terms than are necessary.

Example:



2 AND gate
1 OR gate
1 Inverter

Sum of products expansion is $xyz + xy\bar{z}$

these terms differ only in one variable, and so can be combined

$$xyz + xy\bar{z} = x(y + \bar{y})z = x \cdot 1 \cdot z = xz \rightarrow \text{a Boolean expression with few operators representing the circuit}$$



only one AND gate

- Combining terms in the sum of products expansion leads to a simpler expansion for the circuit.

Minimization of the Boolean function

- produces Boolean sums of Boolean products that represent a Boolean function with:
 - a). fewest products of literals
 - b). each product contains the fewest literals possible.
among all sums of products that represent the Boolean function.
- makes it possible to construct a circuit for this Boolean function that uses:
 - a). fewest gates
 - b). fewest inputs to the AND and OR gates.
in the circuit, among all the Boolean expressions we are minimizing.
- Karnaugh Maps (or K-Maps), 1950
 - useful in minimizing circuits upto six variables
- Quine-McCluskey method, 1960
 - automates the process of minimizing combinational circuits, can be implemented on a computer program.

K-map Method (Graphical), 1953

- visual method for simplifying sum-of-products expansion
- applied only when the function involves six or fewer variables.

K-map with 2 variables → a square of 4 cells

	y	\bar{y}
x	xy	$x\bar{y}$
\bar{x}	$\bar{x}y$	$\bar{x}\bar{y}$

- 4 possible minterms
- 4 cells
- place 1 in a cell if the corresponding minterm representing the cell is in the given Boolean expression

- adjacent cells have minterm that differ in only one literal.

Example: find the K-map for

a. $xy + \bar{x}y$

1	
1	

b. $x\bar{y} + \bar{x}y$

	1
1	

c. $x\bar{y} + \bar{x}y + \bar{x}\bar{y}$

	1
1	1

- identify minterms that can be combined from the K-map
- if two minterms are in two adjacent cells in the K-map, the minterms can be combined to produce a product involving only one variable.

- If 1's in all four cells, the four min-terms can be combined into one term, namely the Boolean expression 1 that involves none of the variables.
- circle blocks of cells in the K-map that represents minterm that can be combined and then find the corresponding sum of products.
- goal is to identify the largest possible blocks and cover all the 1's with fewest blocks using the largest blocks first and always using the largest possible blocks.

Example:

(a) $xy + \bar{x}y$

	y	\bar{y}
x	1	
\bar{x}	1	

$$xy + \bar{x}y = y$$

(b) $x\bar{y} + \bar{x}y$

	y	\bar{y}
x	1	
\bar{x}	1	

(c) $x\bar{y} + \bar{x}y + \bar{x}\bar{y}$

	y	\bar{y}
x	1	1
\bar{x}	1	1

$$x\bar{y} + \bar{x}y + \bar{x}\bar{y} = \bar{x} + \bar{y}$$

K-map with three variables

	yz	$y\bar{z}$	$\bar{y}z$	$\bar{y}\bar{z}$
x	1	2	4	3
\bar{x}	5	6	8	7

one way shown

- think of it as lying as a cylinder
- cell 1, cell 3 adjacent
- cell 5, cell 7 adjacent

To simplify a sum-of-product expansion in 3-variables

- We K-map to identify the blocks of minterms that can be combined
- blocks of two adjacent cells represent pairs of minterms that can be combined a product of literal.
- blocks of 2×2 and 1×1 cell represent minterms that can be combined into a single literal.
- blocks of all 8 cells represents a product of no literals.

Implicant: The product of literals corresponding to a block of 1's in the K-map is called an implicant of the function to be minimized.

Prime Implicant: It is called prime implicant if this block of 1's is not contained in a larger block of 1's representing the product of fewer literals than in this product.

- Goal is to find the largest possible blocks in the map and cover all the 1's in the map with least number of blocks using largest blocks first

Essential Prime Implicant: The largest blocks are always chosen, but we must always choose a block if it is the only block of 1's, covering a 1 in the K-map. Such a block is called an essential prime implicant.

- Covering all the 1's in the map with blocks corresponding to prime implicants, we can express the sum-of-products as a sum of prime implicants.

Note: There may be more than one way to cover all the 1's using the least number of blocks.

Example:

Use K-maps to minimize the sum of product expansions.

$$(a) xy\bar{z} + x\bar{y}\bar{z} + \bar{x}yz + \bar{x}\bar{y}\bar{z}$$

	yz	y \bar{z}	$\bar{y}z$	$\bar{y}\bar{z}$
x		1	1	
\bar{x}	1			1

$$= x\bar{z} + \bar{x}yz + \bar{y}\bar{z}$$

$$(b) x\bar{y}z + x\bar{y}\bar{z} + \bar{x}yz + \bar{x}\bar{y}z + \bar{x}\bar{y}\bar{z}$$

	yz	y \bar{z}	$\bar{y}z$	$\bar{y}\bar{z}$
x			1	1
\bar{x}	1		1	1

∴ minimal expansion into Boolean sums of Boolean products is $\bar{y} + \bar{x}z$

$$(c) x\bar{y}z + xyz + xy\bar{z} + x\bar{y}\bar{z} + \bar{x}yz + \bar{x}\bar{y}z + \bar{x}\bar{y}\bar{z}$$

	yz	y \bar{z}	$\bar{y}z$	$\bar{y}\bar{z}$
x	1	1	1	1
\bar{x}	1		1	1

∴ simplified minimal form is $z + \bar{y} + x$

K-map with four variables : a square divided into 16 cells, representing 16 possible minterms.

One of the ways to form a K-map in 4 variables w, x, y, z

	y_2	$y\bar{2}$	$\bar{y}\bar{2}$	\bar{y}_2
wx	.			✓
$w\bar{x}$				
$\bar{w}\bar{x}$			✓	
$\bar{w}x$	✓	✓	✓	.

- two cells are adjacent iff the minterms they represent differ in one literal
- each cell is adjacent to 4 other cells
- This K-map can be thought of as lying on a torus so that adjacent cells have common boundary.

Simplification Procedure

- Identify those blocks of 2, 4, 8 or 16 cells that represent minterms that can be combined.
- each cell representing a minterm must either be used to form a product using fewer literals or be included in the expansion.

Example

(a) $wxy_2 + wxy\bar{2} + wx\bar{y}\bar{2} + w\bar{y}y_2 + w\bar{y}\bar{y}_2 + w\bar{y}\bar{y}\bar{2} + \bar{w}x\bar{y}_2 + \bar{w}\bar{x}\bar{y}\bar{2}$

	y_2	$y\bar{2}$	$\bar{y}\bar{2}$	\bar{y}_2
wx	1	1	1	
$w\bar{x}$	1		1	1
$\bar{w}\bar{x}$	1	1		
$\bar{w}x$				1

$$= wx\bar{z} + w\bar{x}\bar{y} + \bar{w}\bar{x}y \\ + wy_2 + \bar{w}x\bar{y}z$$

5 implicants, least no. of blocks covering all 1's

OR

	y_2	$y\bar{2}$	$\bar{y}\bar{2}$	\bar{y}_2
wx	1	1	1	1
$w\bar{x}$	1		1	1
$\bar{w}\bar{x}$	1	1		
$\bar{w}x$				1

6 implicants, NOT least no. of blocks covering all 1's

$$(b) w\bar{x}\bar{y}\bar{z} + w\bar{x}y\bar{z} + w\bar{x}y\bar{z} + w\bar{x}\bar{y}\bar{z} + \bar{w}x\bar{y}\bar{z} + \bar{w}\bar{x}y\bar{z} + \bar{w}\bar{x}\bar{y}\bar{z}$$

	$y\bar{z}$	$y\bar{\bar{z}}$	$\bar{y}\bar{z}$	$\bar{y}\bar{\bar{z}}$
$w\bar{x}$			1	
$w\bar{x}$	1	1	1	
$\bar{w}\bar{x}$		1	1	
$\bar{w}x$			1	

$$= \bar{x}\bar{z} + \bar{y}\bar{z} + w\bar{x}y$$

$$(c) wxy\bar{z} + wx\bar{y}\bar{z} + w\bar{x}yz + w\bar{x}\bar{y}\bar{z} + w\bar{x}y\bar{z} + \bar{w}xy\bar{z} + \bar{w}xy\bar{z} \\ + \bar{w}x\bar{y}\bar{z} + \bar{w}x\bar{y}z + \bar{w}\bar{x}y\bar{z} + \bar{w}\bar{x}\bar{y}\bar{z}$$

	$y\bar{z}$	$y\bar{\bar{z}}$	$\bar{y}\bar{z}$	$\bar{y}\bar{\bar{z}}$
$w\bar{x}$			1	1
$w\bar{x}$	1	1	1	
$\bar{w}\bar{x}$		1	1	
$\bar{w}x$	1	1	1	1

$$= \bar{z} + \bar{w}x + w\bar{x}y$$

- Realistic with five or six variables
- Beyond five or six variables, rarely used as K-maps become extremely complicated.
- Concept is very useful to devise new algorithms to minimize Boolean functions implemented in the computer aided design (CAD) program.

Two variable $\xrightarrow{\text{use}} 2 \times 2$ rectangle
 Three variables $\longrightarrow 2 \times 4$ rectangle
 four variables $\longrightarrow 4 \times 4$ rectangle
 n -variables $\longrightarrow 2^{\lceil \frac{n}{2} \rceil} \times 2^{\lceil \frac{n}{2} \rceil}$

- Gray code used to assign a K-map to the minterms

Taking reflexion:

2^3	2^2	2^1
1111	111	11
1110	110	10
1100	100	00
1101	101	01
1001	001	
1000	000	
1010	010	
1011	011	
0011		
0010		
0000		
0001		
0101		
0100		
0110		
0111		

Gray code construction from length n to length $n+1$
 → a reflexion code

4-variables 4×4 , w,x,y,z

	11	10	00	01
11	wx			
10	w̄x			
00	w̄x̄			
01	w̄x			

considering 1st row and last row cells adjacent and 1st column and last column adjacent and using Gray code to label the rows and columns ensures minterms that differ in only one variable are always adjacent.

5-variables 4×8 , w,x,y,z,t

	111	110	100	101	001	000	010	011
11	yzt	ȳzt	ȳz̄t	ȳzt	ȳz̄t	ȳz̄t	ȳz̄t	ȳz̄t
10	w̄x							
00	w̄x̄							
01	w̄x							

↑
take the reflection

- To ensure all cells representing products that differ in only one variable are considered adjacent, verify

- cells in top and bottom cells are adjacent
- 1st and 8th column are adjacent
- 1st and 4th column are adjacent
- 5th and 8th column are adjacent
- 2nd and 3rd, 3rd and 6th are adjacent.

Use of K-maps to minimize a Boolean function in n -variables

- Draw a K-map of the appropriate size
 - Place 1s in all cells corresponding to minterm in the sum of product expansion of this function
- Identify all prime implicants of the Boolean function
 - look for the blocks consisting of 2^k clustered cells containing a 1, where $1 \leq k \leq n$
 - these blocks correspond to the product of $n-k$ literals.
 - a block of 2^k cells each containing a 1 not contained in a block of 2^{k+1} cells each containing 1 is a prime implicant
 - as no product obtained by deleting a literal is also represented by a block of cells all containing 1

-
- K-map containing 2^n cells (i.e. n variables)

Use a rectangle containing $2^{\lceil \frac{n}{2} \rceil}$ rows and $2^{\lfloor \frac{n}{2} \rfloor}$ columns

$$\left(\lceil \frac{n}{2} \rceil + \lfloor \frac{n}{2} \rfloor = n \right)$$

- Once all prime implicants have been identified, the goal is to find the smallest possible subset of these prime implicants, with the property that: the cells representing these prime implicants cover all the cells containing a 1 in the K-map
 - first select the essential prime implicants, as each of these is represented by a block that covers a cell containing a 1 that is not covered by any other prime implicant
 - add additional prime implicants to ensure that all 1s in the K-map are covered. (This step can become exceedingly complicated for larger number of variables)

Don't Care Conditions

- Some circuits care about only output for some combinations of input values
- Other combinations of input values are not possible or never occur
- This gives us freedom in producing a simple circuit with the desired output
- The output values for all those combinations that never occur can be arbitrarily chosen
- The values of functions for these combinations are called don't care conditions.

- A d is used in K-map to mark those combinations of values of the variables for which the function can be arbitrarily assigned.
- In the minimization process, we can assign 1 as values of those combinations of input values that lead to the largest blocks in the K-map.

Example: BCD (Binary Coded Decimal)

Digit	BCD codeword	
0	0 0 0 0	0
1	0 0 0 1	0
2	0 0 1 0	0
→ 3	0 0 1 1	0
4	0 1 0 0	0
5	0 1 0 1	1
6	0 1 1 0	1
→ 7	0 1 1 1	01
→ 8	1 0 0 0	1
9	1 0 0 1	1
	w x y z	f

$873 \rightarrow 1000\ 0111\ 0011$

6 combinations out of 16 never used to encode digits

Question:

Suppose that a circuit is built that produces an output of

$$\begin{cases} 1 & \text{if the decimal digit is } \geq 5 \\ 0 & \text{if the decimal digit is } < 5 \end{cases}$$

How can this circuit be simply built using OR gate, AND gate and inverters?

$$F = \bar{w}x\bar{y}z + \bar{w}xy\bar{z} + \bar{w}xyz + w\bar{x}\bar{y}\bar{z} + w\bar{x}\bar{y}z$$

The K-map for F , with d in the don't care positions.

	y_2	$y_2 \bar{}$	$\bar{y}_2 \bar{}$	\bar{y}_2
wx	d	d	d	d
$w\bar{x}$	d	d	1	1
$\bar{w}\bar{x}$				
$\bar{w}x$	1	1		1

$$f = w\bar{x}\bar{y} + \bar{w}xy + \bar{w}x^2$$

	y_2	$y_2 \bar{}$	$\bar{y}_2 \bar{}$	\bar{y}_2
wx	d	d	d	d
$w\bar{x}$	d	d	1	1
$\bar{w}\bar{x}$				
$\bar{w}x$	1	1		1

$$f = w\bar{x} + \bar{w}xy + x\bar{y}^2$$

	y_2	$y_2 \bar{}$	$\bar{y}_2 \bar{}$	\bar{y}_2
wx	d	d	d	d
$w\bar{x}$	d	d	1	1
$\bar{w}\bar{x}$				
$\bar{w}x$	1	1		1

$$f = w + xy + xz^2$$

simplest possible sum of product expansion


Exercise:

Simplify the Boolean function $f(w,x,y,z) = \sum(1,3,7,11,13)$ and the don't care condition $d(w,x,y,z) = \sum(0,2,5)$

- Is placed in the sequences of the map represents the minterm of F
- the minterms not included in F , denote the compliment \bar{F} of F
- complement \bar{F} of F is represented in the map by a square not marked 1
- mark empty squares by 0s and combine them into valid adjacent squares
 \rightarrow Get a simplified expression of \bar{F} of F
- Then apply DeMorgan's laws to \bar{F} to get F back

Example: $F = \Sigma \{0, 1, 2, 5, 8, 9, 10\}$

wz	00	01	11	10
00	1 ₀	1 ₁	1 ₃	1 ₂
01	1 ₄	1 ₅	1 ₉	1 ₆
11	1 ₁₂	1 ₁₃	1 ₁₅	1 ₁₄
10	1 ₈	1 ₉	1 ₁₁	1 ₁₀

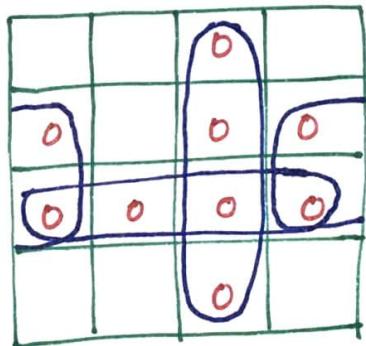

$$\begin{aligned}\bar{f} &= \bar{y}\bar{z} + \bar{w}\bar{z} + \bar{x}\bar{z} \\ f &= (y+z)(w+x)(x+z)\end{aligned}$$

- Unfortunately, minimizing Boolean function with many variables is a computationally intensive problem
 - NP-complete problem
 - No polynomial time algorithm for minimizing Boolean circuits so far
- Quin-McCluskey's method → exponential complexity and only used when # literals ≤ 10
- So far, the best algorithm minimizes only circuits with no more than 25 variables
- Heuristic methods → used to substantially simplify Boolean expressions with a large number of literals.
 - not necessarily minimize

The Quine-McClusky Method (1950)

- can be used for Boolean functions in any number of variables
- Two points
 - (i) find those terms that are candidates for inclusion in a minimal expansion as a Boolean sum of Boolean products
 - (ii) determine which of these terms to actually use

Example: Show how the Quine-McCluskey method can be used to find a minimal expansion equivalent to

$$xyz + x\bar{y}z + \bar{x}yz + \bar{x}\bar{y}z + \bar{x}\bar{y}\bar{z}$$

(i)

minterms	bitstring	# of 1's	
1. xyz	111	3	(1,2)
2. $x\bar{y}z$	101	2	(1,3)
3. $\bar{x}yz$	011	2	(2,4)
4. $\bar{x}\bar{y}z$	001	1	(3,4)
5. $\bar{x}\bar{y}\bar{z}$	000	0	(4,5)

- minterms that can be combined are those that can be differ in exactly one literal
- Hence, two terms that can be combined differ by exactly one in the # of 1's in the bitstring.

- When two minterms are combined into a product, this product contains two literals.
- A product in two literals is represented using a dash to denote the variable that does not occur.

Step 0	Bit Strings	Step 1	Term	Bit Strings	Step 2	Term	Bit Strings.
xyz	111		x_2	1-1		z	- - 1
$x\bar{y}z$	101		y_2	-11			
$\bar{x}yz$	011		\bar{y}_2	-01			
$\bar{x}\bar{y}z$	001		\bar{x}_2	0-1			
$\bar{x}\bar{y}\bar{z}$	000		$\bar{x}\bar{y}$	00-			

- Next, all pairs of products of two literals that can be combined are combined into one literal

Two such products can be combined if they contain literals for the same two variables, and literals for only one of the two variables differ.

- (ii) To identify a minimal set of products needed to represent the Boolean function.

- Note that the above table indicate which terms have been used to form products with fewer literals (1,2,3,4). These terms will not be needed in a minimal expansion
- Begin with all those products that were not used to construct products with fewer literals.

Cover finding Table

candidate product

	1	2	3	4	5
$\bar{x}y\bar{z}$	x	x	x	x	
$\bar{x}\bar{y}2$				x	x
z					
$\bar{x}\bar{y}$					

- Form a table which has a row for each candidate product formed by combining original terms of a column for each original term.
- Put an x in a position if the original term in the sum-of-product expansion was used to form the candidate product
- In this case, the candidate product is said to **cover** the original minterm, (e.g. $\bar{x}\bar{z}$ covers $\bar{x}y\bar{z}$ and $\bar{x}\bar{y}\bar{z}$)
- need to include atleast one product that covers each of the original minterms
- Only one x in a column in the table \rightarrow corresponding product in the row of this x must be used.
- From the above table, see that both z and $\bar{x}\bar{y}$ are needed

Hence, the final answer is $z + \bar{x}\bar{y}$

Sequence of steps to simplify a sum-of-products expression in the Quine-McCluskey method

1. express each minterm in n variables by a bit string of length n while
 - 1 in the i^{th} position if x_i occurs
 - 0 in the i^{th} position if \bar{x}_i occurs
2. group the bit strings accordingly to the # of 1's in them
3. determine all products in $n-1$ variables that can be formed by taking the Boolean sum of minterms in the expansion
 - minterms that can be combined are represented by bit strings that differ in exactly one position
 - represent these products in $n-1$ variables with strings that have
 - 1 in the i^{th} position if x_i occurs in the product
 - 0 in the i^{th} position if \bar{x}_i occurs in the product
 - (dash) in the i^{th} position if there is no literal involving of x_i in the product
4. Determine all products in $n-2$ variables that can be formed by taking the Boolean sum of products in $n-1$ variables found in the previous step.
 - products in $n-1$ variables that can be combined are represented by bit strings that have a dash in the same position and differ in exactly one position

5. Continue combining Boolean products into products with fewer variables as long as possible
6. find all the Boolean products that arose that were not used to form a Boolean product in one fewer literal
7. find the smallest set of these Boolean products such that the sum of these products represents the Boolean function
 - done by forming a table showing which minterms are covered by which products
 - every minterm must be covered by at least one product
 - first find all essential prime implicants
 - An essential prime implicant is the only prime implicant that covers one of the minterms
 - Then simplify the table by eliminating the columns for minterms covered by this prime implicant
 - eliminate any prime implicants that cover a subset of minterms covered by another prime implicant.

(e.g. $\bar{x}yz$ can be ignored while $w\bar{y}z$ is included together with $\bar{w}z$ and $w\bar{y}z$ as:
 $\bar{x}yz$ covers $\{w\bar{y}z, w\bar{y}z\}$

- eliminate column for a minterm if there is another minterm that is covered by a subset of the prime implicants that cover this minterm
 (e.g. minterm $\bar{w}\bar{x}yz$ can be ignored, $\bar{w}\bar{x}y$ is covered by prime implicants $\bar{w}z$ and $\bar{x}y$)
 Let 'm' be a minterm covered by 'c', then if \exists another minterm 'm' with $c' \subseteq c$, delete column for m.)
- This process of
 - (a) identifying essential prime implicants that must be included,
 - (b) eliminating redundant prime implicants (i.e. eliminating dominated rows), and
 - (c) identifying minterm that can be ignored (i.e. eliminating dominating columns)
 is iterated until the table does not change
- Finally, use a backtracking procedure to find the optimal solution, when we add prime implicants to the cover to find possible solutions.
- Finding cover is NP-complete problem

Example

$$wy\bar{z} + w\bar{y}z + w\bar{z}y\bar{z} + \bar{w}xyz + \bar{w}x\bar{y}z + \bar{w}\bar{x}yz + \bar{w}\bar{x}\bar{z}y$$

Step 0		Step 1		Step 2	
Terms	Bit strings	Terms	Bit strings	Terms	Bit strings
1. $wxyz$	1110 (5) (1,3)	2. $w\bar{y}z$	1-10 (6,8,4,5)	3. wz	0-1
2. $w\bar{y}z$	1011 (3) (1,5)				
3. $w\bar{z}y\bar{z}$	1010 (2) (4,6)				
4. $\bar{w}xyz$	0111 (5) (2,3)	5. $w\bar{y}$	101-		
5. $\bar{w}x\bar{y}z$	0101 (2) (2,5)	6. $\bar{z}y\bar{z}$	-011		
6. $\bar{w}\bar{x}yz$	0011 (2) (2,6)	7. $\bar{w}\bar{x}z$	00-1		
7. $\bar{w}\bar{x}\bar{y}z$	0001 (1) (6,7)				
	(4,5)				
	(4,5)	8. $\bar{w}x2$	01-1		
	(4,6)	9. $\bar{w}yz$	0-11		
	(5,6)	10. $\bar{w}\bar{y}2$	0-01		

	1	2	3	4	5	6	7
1. $w\bar{y}z$	x						
2. $w\bar{y}z$		x					
3. $w\bar{z}y\bar{z}$			x				
4. $\bar{w}xyz$				x			
5. $\bar{w}x\bar{y}z$					x		
6. $\bar{w}\bar{x}yz$						x	
7. $\bar{w}\bar{x}\bar{y}z$							x

final answer: $\bar{w}2 + w\bar{y}2 + w\bar{z}y$
or

$$\bar{w}2 + w\bar{y}2 + \bar{z}yz$$